

Control Design of PWM Converters: The User Friendly Approach

Prof. Sam Ben-Yaakov

Email: sby@ee.bgu.ac.il;

Web: <http://www.ee.bgu.ac.il/~pel/>

Seminar material download: PET06

**Power Electronics Technologies Conference
Long Beach CA, October 2006**

© All rights reserved. Duplication or copying is not permitted
without written permission by author

Motivation

- Most switch mode systems need to operated in closed loop
- Performance largely dependent on the Compensator (feedback) design
- Loop control design is conceived as “black magic” OR requiring tedious analytical derivations
- Digital control is becoming relevant

Objective


- To present a user friendly version of control loop design including both analog and digital control
- Based on:
 - ✓ Intuition
 - ✓ Simulation
 - ✓ Simple calculations

Outline

1. Basics of feedback theory and graphical representation
2. Relationship between LoopGain and dynamic response
3. PWM converters as feedback systems
4. Voltage Mode (VM) control
5. Current Mode (dual loop) control
6. Simulation tools
7. Average models
8. Analog compensator networks
9. Digital control
10. Q&A

 1. Basics of feedback theory and graphical representation

Block diagram of a feedback systems (one loop)




$$A_{CL} = \frac{S_o}{S_{in}} = \frac{A_{OL}}{1 + \beta \cdot A_{OL}}$$

$$LG \equiv \beta A_{OL}$$

$$\left. \frac{S_o}{S_{in}} \right|_{\beta \cdot A_{OL} \gg 1} = \frac{1}{\beta}$$


$$\left. \frac{S_o}{S_{in}} \right|_{\beta \cdot A_{OL} \ll 1} = A_{OL}$$

Block Diagram

 

$$A_{CL} = \frac{S_o}{S_{in}} = \frac{1}{1 + \underbrace{H_2 H_1 K P}_{LG(f)}}$$


Effect of Feedback

 


$$A_{CL} = \frac{S_o}{S_{in}} = \frac{P}{1 + \underbrace{H_2 PK}_{LG(f)}}$$

$$A_{CL}|_{LG(f) \gg 1} = \frac{1}{H_2 K}$$



PWM Converter

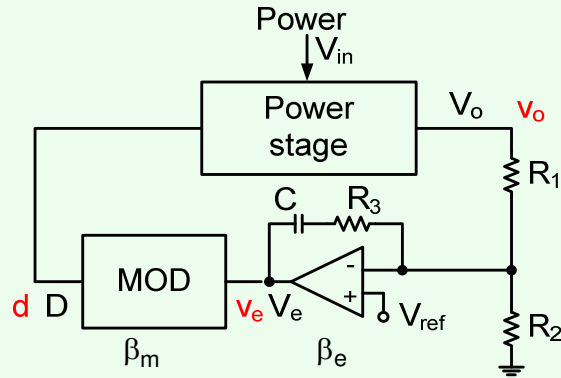

Block diagram concepts

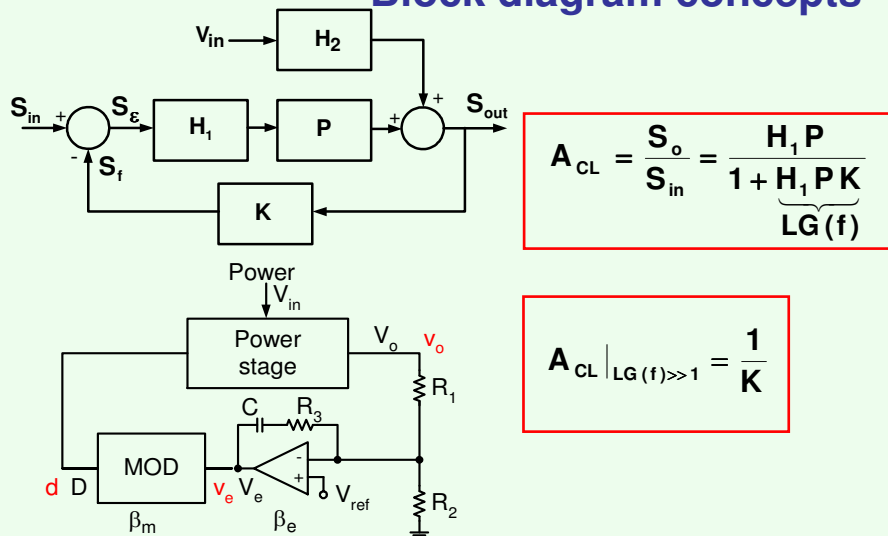


Audio susceptibility

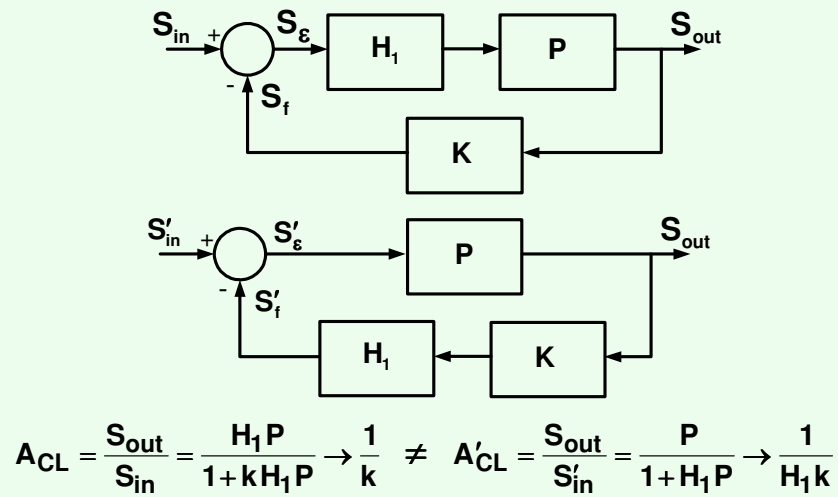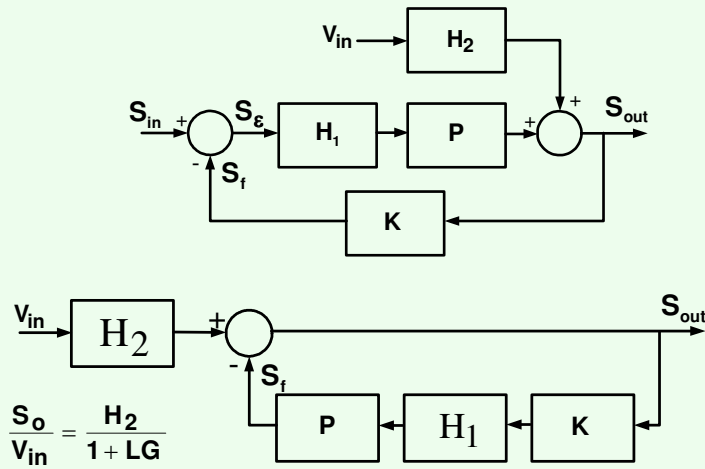

But loop gains are equal: $LG(f) = H_1 K P$

Block diagram division

 


$$LG(f) = AB$$

A – known (power stage + divider)


B – unknown (have to be designed)

 Graphical representation of BA conventional method




- Tedious – need to re-plot BA
- Analysis (not design) oriented
- Requires iterations

Graphical Representation of BA

 

Stability of Feedback System
 
$$H(s) = \frac{b_m s^m + b_{m-1} s^{m-1} + \dots + 1}{a_n s^n + a_{n-1} s^{n-1} + \dots + 1}$$




- RHP solutions include the term $\sin(\omega t)e^{\alpha t}$

Stability Criterion

$$A_{CL} = \frac{H_1 K}{1 + LG(f)}$$


- The system is unstable if $\{1 + LG(f)\}$ has roots in the right half of the complex plane.
- Nyquist criterion is a test for location of $\{1 + LG(f)\}$ roots.
- Nyquist criterion is normally translated into the Bode plane (frequency domain)

Nyquist

 


- Stable

Nyquist

 


- Oscillatory

Nyquist

 


- Unstable
- The culprit: Phase Lag
- Phase Lead in LG can help stabilize a system


Bode plane

 


Bode plane

 

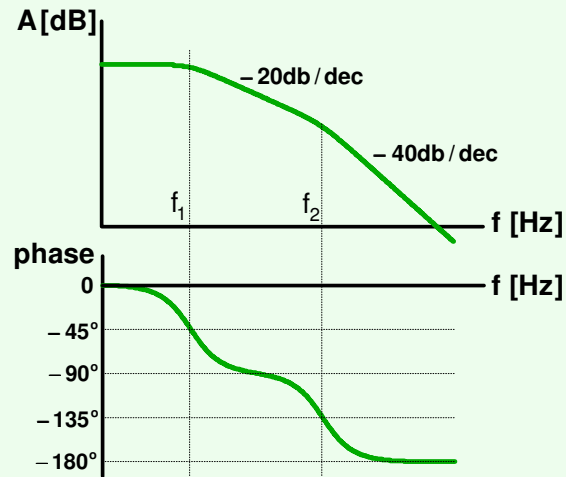Minimum Phase Systems no Right Half Plane Zero (RHPZ)




 Rate of closure (ROC) (minimum phase systems)




$$BA = \frac{\left(1 + j\frac{f}{f_1}\right) \cdot \left(1 + j\frac{f}{f_2}\right) \cdot \left(1 + j\frac{f}{f_3}\right) \cdots}{\left(1 + j\frac{f}{f_1}\right) \cdot \left(1 + j\frac{f}{f_2}\right) \cdot \left(1 + j\frac{f}{f_3}\right) \cdots} = \frac{k}{\left(1 + j\frac{f}{f_p}\right)}$$

 Application of the $1/B$ curve Rate of closure




- Rate of closure of BA is the difference between the A and B slopes
- No need to re-plot BA
- Design oriented approach

Stability Criterion

 


If rate of closure -20 dB/dec system is stable

Phase Margin Examples

 


Phase Margin Calculation

 


- For minimum phase systems history is not important

Approximate Phase Margin Calculation

 


- Get the accurate phase at intersection by **simulation**

Design Steps

 


- Draw A
- Select cross point of BA (\ll than $f_s/2$, for PWM)
- Select B shape

Stability of a Source-Load System

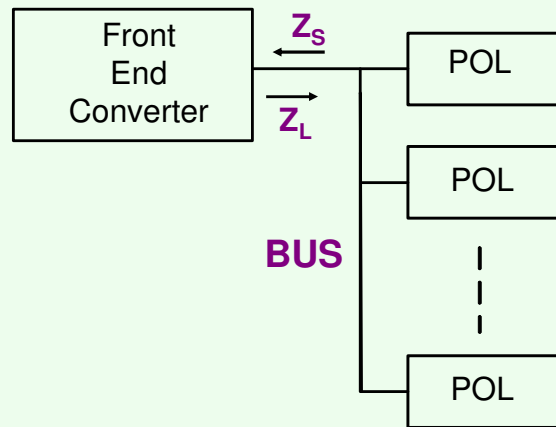

- $Z_L \rightarrow$ negative resistance

System stability

 


$$\text{LoopGain} = \frac{1}{Z_S} Z_L$$

Convenient way to examine the LG stability is the Nyquist stability test

2. Relationship between Loop Gain and dynamic response

Response in Closed Loop

 

$$\text{Desired: } A_{CL} = \frac{1}{K}$$



$$\text{What we get: } A_{CL} = \frac{1}{K} \cdot \frac{1}{\frac{s^2}{\omega_0^2} + \frac{s}{\omega_0 Q} + 1} \quad \text{for } \varphi_m \leq 50^\circ$$

$$A_{CL} = \frac{1}{K} \cdot \frac{1}{\frac{s}{\omega_0} + 1} \quad \text{for } \varphi_m \geq 50^\circ$$


$$A_{CL}(0) = \frac{1}{K}$$

- For small φ_m , A_{CL} behaves as a second order system

  Overshoot and Q in Closed Loop in Response to step in S_{in}



 
$$Q \cong \frac{\sqrt{\cos \phi_m}}{\sin \phi_m} \quad \text{for } \phi_m < 50^\circ$$




Design target $\phi_m \geq 45^\circ$

Load-Step Response

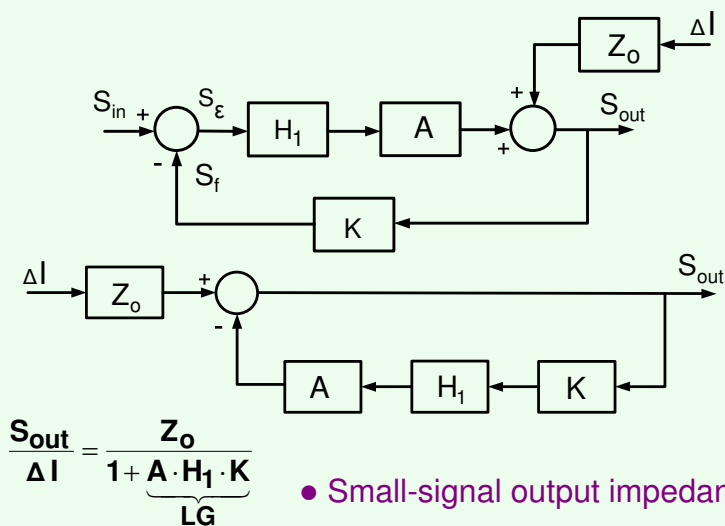



Load-Step Response

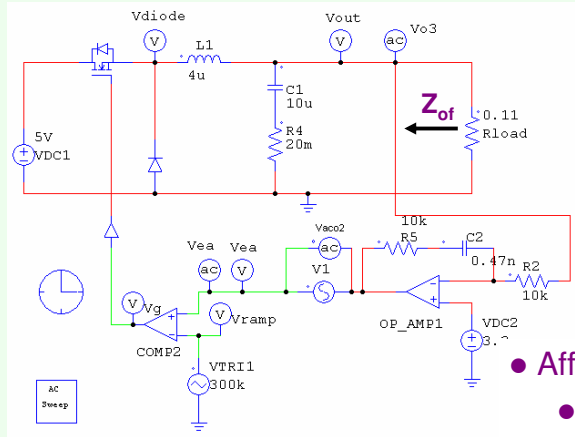

• Affected by:

- Output impedance
- ESR of output capacitor
- Slew rate of inductor

  
Output Impedance (Immunity to load changes)



$$Z_{of} = \frac{v_{out}}{\Delta i_o} = \frac{Z_o}{1 + \frac{AB}{LG}}$$

• Buck converter – small signal

 
Audio-Susceptibility (Line Regulation) (Immunity to input voltage changes)



$$\frac{V_{out}}{V_{in}} = \frac{H_2}{1 + LG(f)}$$

- Large LG reduces susceptibility

Steady-state (DC) Error

 

$$S_{\epsilon} = \frac{S_{in}}{1 + LG}$$


- S_{ϵ} is the offset between the sampled output and reference
- Small DC error for large $LG(0)$

Dynamic Response Summary

- Systems that have a slope of -20 db/dec are easy to control
- Response is largely determined by $LG(f)$
- Desired LG:
 - LG as large as possible at low frequencies
(small DC errors)
 - LG of large BW - intersection point of A and $1/B$
(quick response, fast recovery, rejection of V_{in} changes)
 - Phase margin $> 45^\circ$
(reasonable overshoot)

The culprit: Phase delay in LG

Nyquist

 


Design target $\phi_m \geq 45^\circ$

3. PWM converters as feedback systems

Issues:

- Stability
- Rejection of input voltage variations (audio susceptibility)
- Immunity to load changes
- Quick response to reference change - good tracking.


PWM converter in closed loop

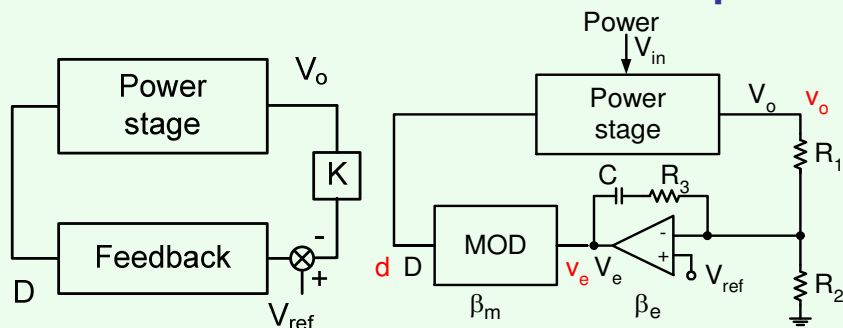

- Small signal responses
- Linearization around operating point

Type of Blocks

Small Signals (Perturbation) Responses

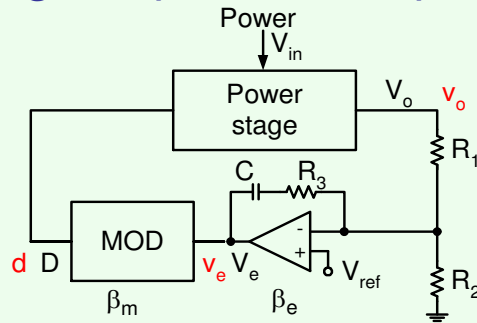


- Power stage is a Switching System (may be non linear)
- Feedback is an analog or digital controller
- Modulator: mixed mode
- Linear control theory based design → small signal response

Small-Signals (Perturbation) Responses


- Analytical solutions
- Simulation
 - Injection of sinusoidal perturbation
 - AC analysis of behavioral average model

• **This seminar promotes the simulation approach**

Small signal response of the modular



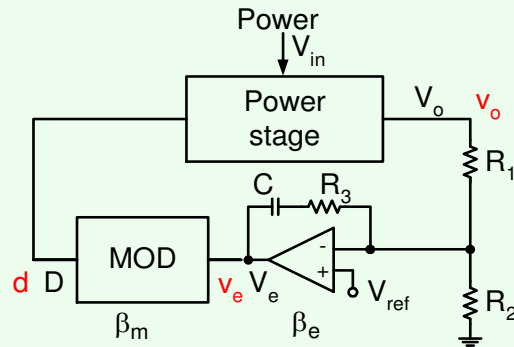


 • Relationship between v_e and d ($K_m = d/v_e$)



d is the AC component of D

Modulator

   

$$V_t = \frac{(V_p - V_v)t}{T_s} + V_v$$


$$V_t = V_e = \frac{(V_p - V_v)t_{on}}{T_s} + V_v$$

$$\frac{t_{on}}{T_s} = D_{on} = \frac{(V_e - V_v)}{V_p - V_v}$$

$$d = \frac{v_e}{V_p - V_v} = \frac{v_e}{V_a}$$

$$K_m = \frac{d}{v_e} = \frac{1}{V_a}$$

THE CONTROL DESIGN PROBLEM

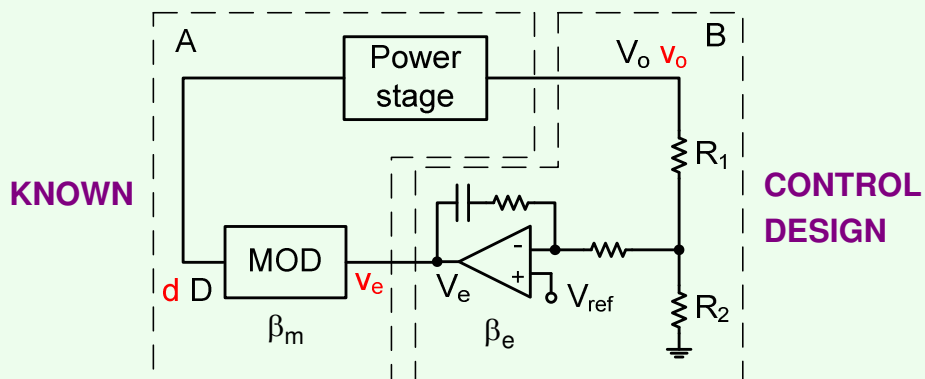


$$\frac{V_o(f)}{V_e} - \text{Analog Function} \quad \beta_m = \frac{d}{v_e}$$


- A → Power Stage ; B → compensator

4. Voltage mode (one loop) control


Block diagram

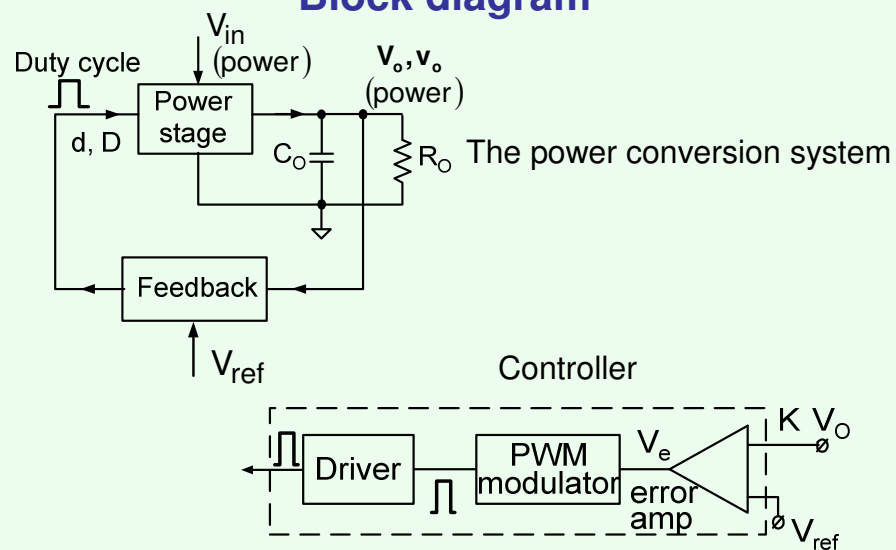


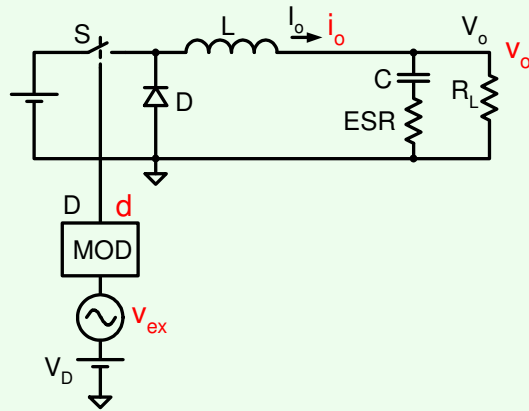
Buck small-signal frequency response (CCM)



Buck frequency response (CCM)

 

  
- Second order plus zero due to ESR of C_o



Buck Derived Converters


- Forward
 - Half bridge (HB)
 - Full Bridge (FB)
-
- **Simulation is the simplest way to obtain the transfer functions**

Boost Power Stage Small signal response

 


- **RHPZ – non minimum-phase system**

CM Boost

 

Buck-Boost (Flyback) Power Stage

 


•RHPZ – non minimum-phase system

5. Current Mode (dual loop) control


Current Feedback

- The problem of voltage mode control:
Transfer function is second order
- Solution: Add current Feedback
- **System order is reduced for each state variable (inner loop) feedback**


The effect of current feedback

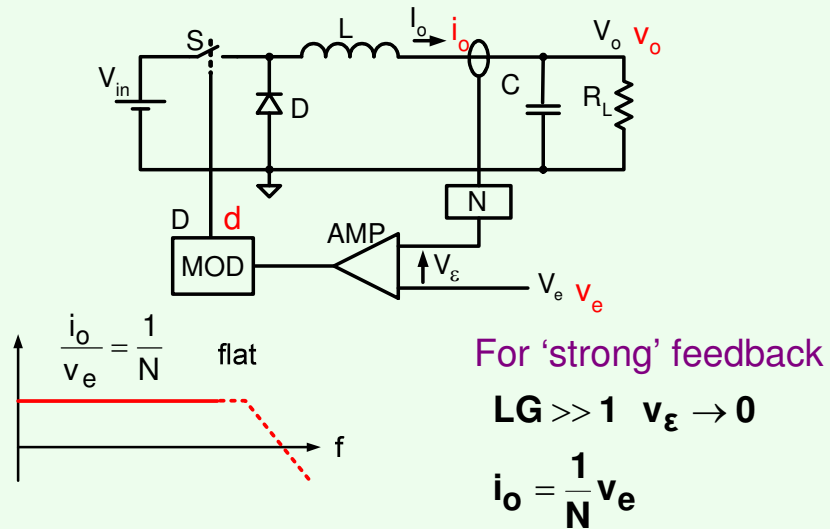

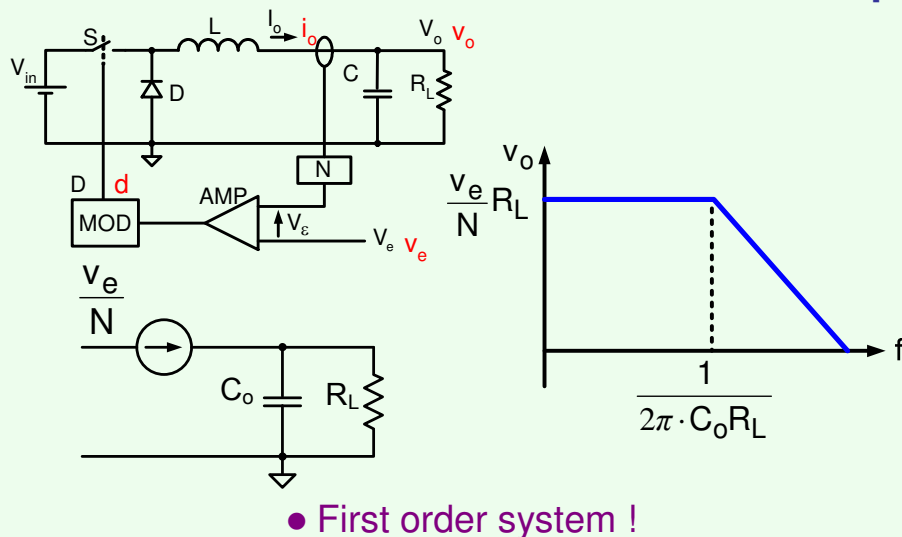
Transfer function with closed Current Loop



Current Mode

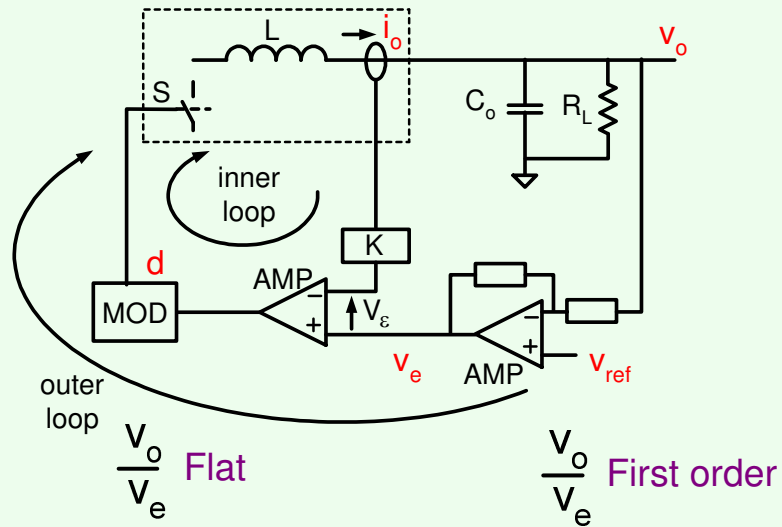

The advantages of current feedback

 


Typical power stage
VM

Same power stage
(outer loop) with
CM


7. Peak Current Mode (PCM) control

PCM Modulator

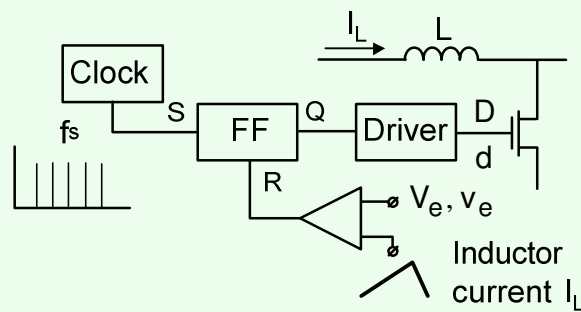


$$\frac{V_o}{V_{in}} = f(D_{on}) \text{ is the same !}$$

Implementation CM Boost

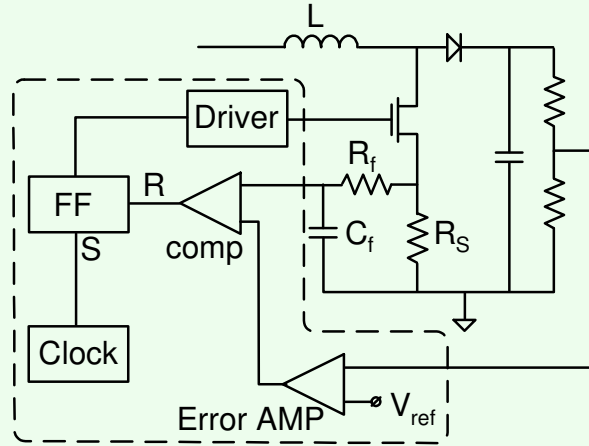


Some controllers have amplifiers for sensed current

The nature of Subharmonic Oscillations

 

The geometric explanation
 
$$D < 0.5 \quad \Delta I_2 < \Delta I_1$$




$$D > 0.5 \quad \Delta I_2 > \Delta I_1$$

•For $D > 0.5$ need slope compensation

Extra delay in PCM (Ridley)

- PCM is a current sampling process
- Subject to sampling delay
- Delay was derived by Ray Ridley
- Important for frequencies above $f_s/10$
- Mostly of theoretical importance

Average Current Mode (ACM) Block diagram

 

- Current sample is filtered first attenuate high frequency (f_s)

PCM and ACM

- Both are current feedbacks
- Both reduce the order of system
- The difference is in BW of the current feedback loop
- Both increase the output impedance

Advantages of peak CM (PCM)

- * Cycle by cycle protection
- * Better dynamics

Disadvantages

- * Leading edge spike
- * Subharmonic oscillations


6. Simulation tools

- General purpose simulators
- Dedicated simulators
- PC and web based simulators
- **This seminar promotes PC based general purpose simulators**

Why Simulation

- Most control design methods apply graphical representations of transfer functions
- One can get the plots from analytical expressions or by simulation
- Simulation is the easiest way to get “A” (the **small signal** response of the power stage)

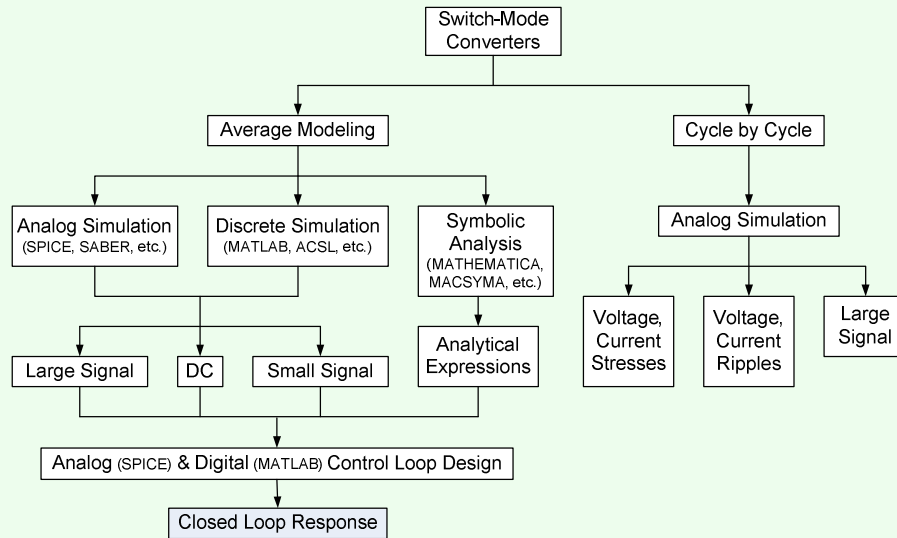Computer Simulation of Power Conversion Systems



Desired Simulator's Features for Power Electronics Systems

- Convergence
- Physical models
- Small signal analysis
- Interfaces
- Run time
- Behavioral models
- Statistical and optimization analysis
- Discrete domain simulation capabilities

Some Popular Modern Simulators

SPICE Based (Berkeley)

- PSPICE – MicroSim - Orcad - Cadence
- ICAP/4 – Intusoft
- MICROCAP - Spectrum

Others

- PSIM - Powersim
- Simplorer -Ansoft
- PLECS -Plexim


Power IC Models Library

- AEi – Design Automation

PSPICE – The Physical Simulator

- Most popular
- SPICE based simulator (Berkley)
- Used extensively for circuit simulation
- Extensive physical models libraries
- Behavioral models (ABM)
- AC analysis
- Statistical analysis
- Optimization tool
- Some PWM models
- MATLAB/Simulink interface

Working with PSPICE

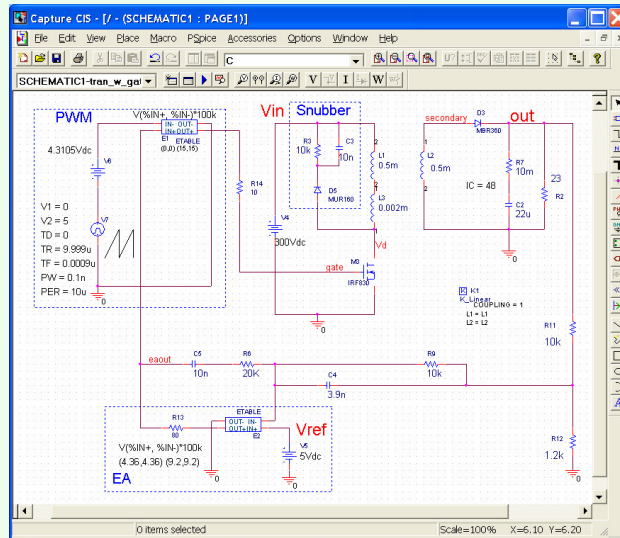

PSPICE Convergence Problems

ERROR -- Convergence problem in transient analysis at Time = 201.9E-06
Time step = 1.391E-15, minimum allowable step size = 5.000E-15

These devices failed to converge:
M1

ERROR -- Discontinuing simulation due to convergence problem

Last node voltages tried were:

NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE	NODE	VOLTAGE
(VD)	348.4900	(OUT)	47.9820	(EAOOUT)	4.7044	(NO4759)	300.0000

PSPICE Runtime Settings

	Use Original Value	Change To	
Relative accuracy of V's and I's:	<input type="checkbox"/> 0.001	<input type="checkbox"/> 0.001 (RELTOL)	OK
Best accuracy of currents (amps):	<input type="checkbox"/> 1e-012	<input type="checkbox"/> 1e-012 (ABSTOL)	OK & Resume Simulation
Best accuracy of voltages (volts):	<input type="checkbox"/> 1e-006	<input type="checkbox"/> 1e-006 (VNTOL)	Cancel
Minimum conductance for any branch (1/ohm):	<input type="checkbox"/> 1e-012	<input type="checkbox"/> 1e-012 (GMIN)	Help
Run to time (seconds):	<input type="checkbox"/> 0.005	<input type="checkbox"/> 0.005 (TSTOP)	
Maximum step size (seconds):	<input type="checkbox"/>	<input type="checkbox"/> (TMAX)	
DC and bias "blind" iteration limit:	<input type="checkbox"/> 150	<input type="checkbox"/> 150 (ITL1)	
DC and bias "best guess" iteration limit:	<input type="checkbox"/> 20	<input type="checkbox"/> 20 (ITL2)	
Transient time point iteration limit:	<input type="checkbox"/> 10	<input type="checkbox"/> 10 (ITL4)	

- Very common in switched circuits simulation


AEi Power IC Library

- PWM controllers are not included in PSPICE libraries
- AEi's library supports Power Electronics
 - *150 SPICE Models for Popular Power ICs*
 - ✓ *Regulators, Controllers, Switchers*
 - ✓ *FET Drivers*
 - *Support for Capture and Schematics*
 - ✓ *Symbols*
 - ✓ *Example Applications schematics/simulations*
 - ✓ *Documentation*

PSIM -The Switching Circuit Simulator

- Disregards switching instances
 - Fast and effective time domain algorithm
 - Constant time step approach
 - Transient (time domain) based AC analysis
 - User friendly intuitive interface
 - Generic models: passive, switchers, motors
 - Analog Behavior Models library
 - Simulink interface
 - Interface to magnetics program
-
- Prone to errors in simulation results
 - Simple output graphics utility

PSIM AC Model

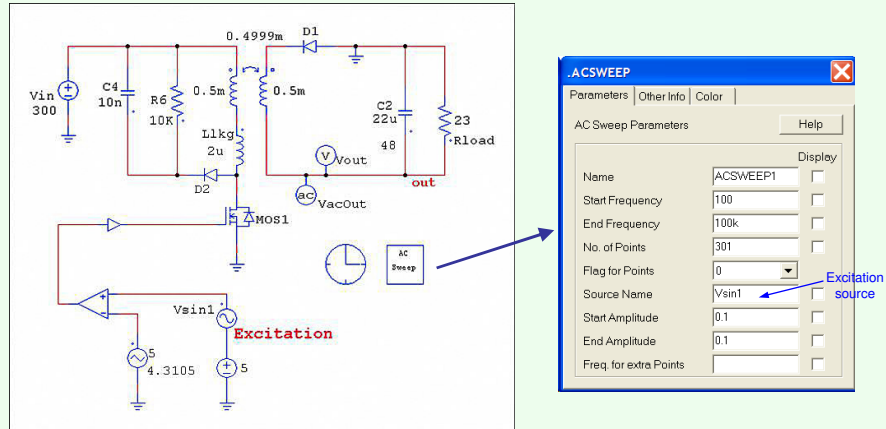


- Multiple time-domain runs are used to obtain AC response


PLECS – The MATLAB Plug-In

- Power tool-kit for SIMULINK
- Allows the simulation of power stage as integrated part of MATLAB (SIMULINK) simulation without introducing extra delays
- Ideal for investigating digital control loops in power systems
- Only generic models
- Simulink interface for both schematic and graphics

PLECS Circuit as a Simulink Block

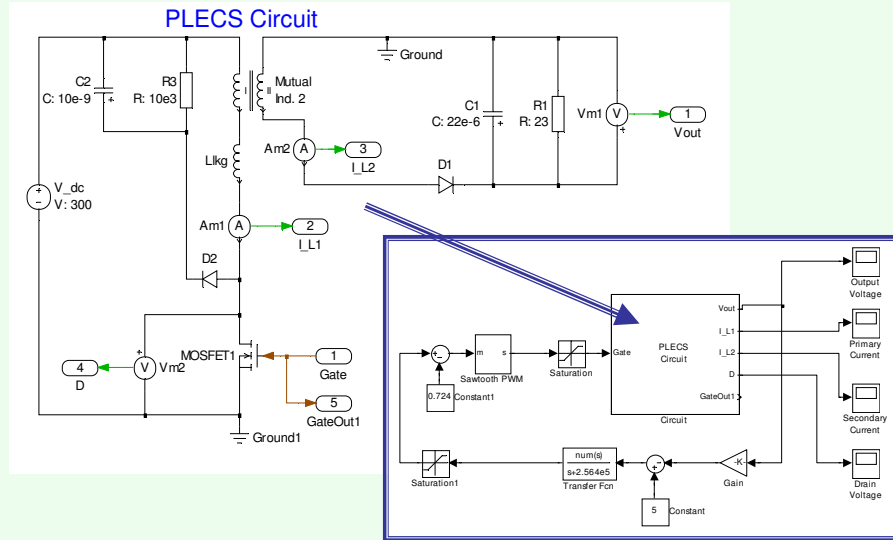


PSPICE cycle-by-cycle model

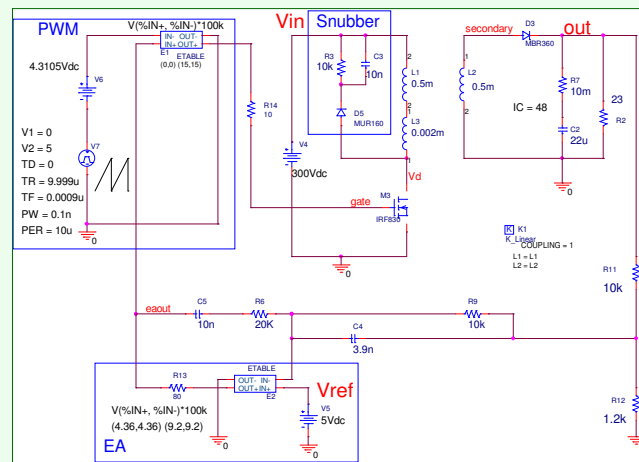


PSIM Flyback cycle-by-cycle model (Time Domain)

Demo
Real time: 3 ms

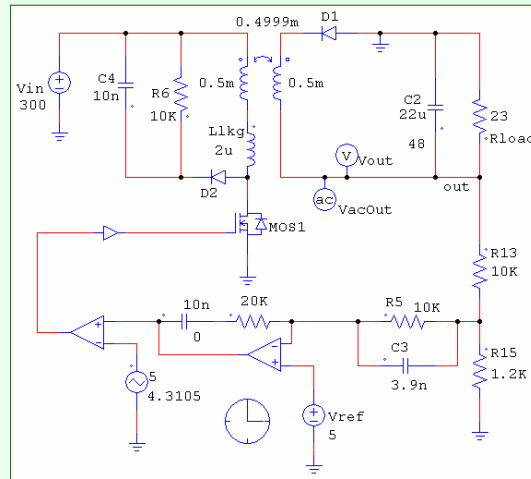

 
PSIM DCM cycle-by-cycle simulation results




$R_{load}=220\Omega$

- Textbook waveforms

 PSPICE vs. PSIM Flyback cycle-by-cycle simulation results



 PSPICE vs. PSIM Flyback cycle-by-cycle simulation results



Small Signal (AC) Analysis (Needed for Control Design)

Two Alternatives:

1. Full switched circuit:

Injection of a sinusoidal perturbations

PSPICE → manually

PSIM → automatic


2. Average Model

PSPICE → AC analysis

(linearization by simulator)


PSIM → automatic transient injection

 Small signal response by injection of sinusoidal perturbations (time domain)




• Transient simulation – any simulator


PSIM Realization (Buck)

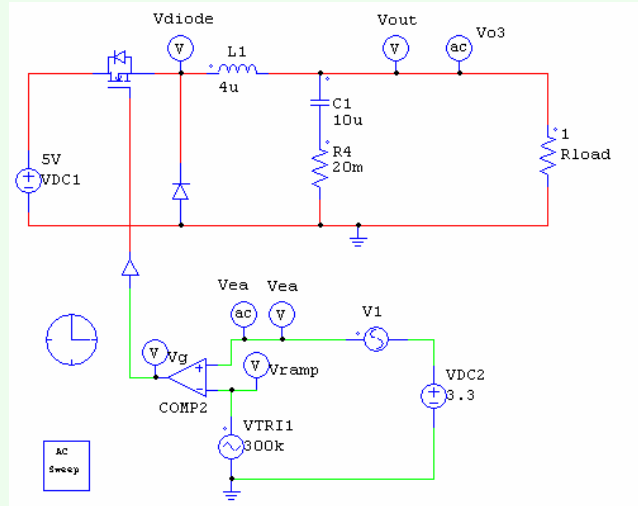

 Power-Stage small signal transfer function By injection of sinusoidal perturbation - PSIM & PSPICE




Boost

 

PSPICE

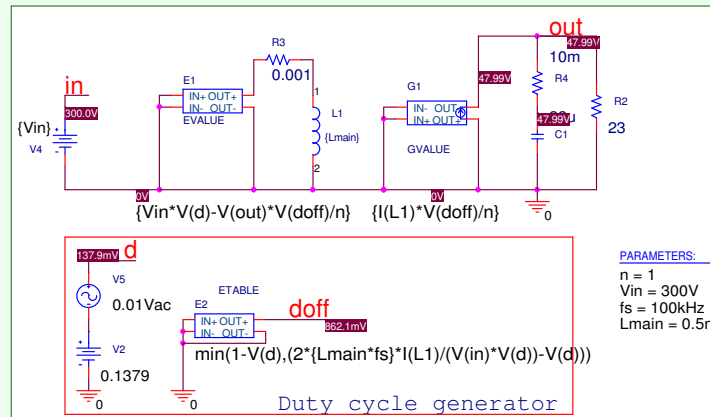The Behavioral Approach Average Model of Flyback - PSPICE




- Average models can be applied to obtain frequency response – AC analysis (to be discussed later)

Signal injection versus Average model

- Signal injection
 - Applies the switching schematics as is
 - Takes a long time to run
 - Noisy at high frequency
- Average model
 - Runs very fast
 - Need to built a behavioral equivalent
 - Some topologies/controllers are not easy to convert to average circuits

PSIM vs. PSPICE AC Comparison

$$\frac{V_{out}}{d}$$

 

Behavioral average modeling of switch mode systems

Applications:

- DC transfer functions
- Transient (large signal, time domain) phenomena
- Small signal (AC, time domain) transfer functions

Not applicable to:

- Switching details, rise and fall times, spikes
- Device characteristics and losses
- Subharmonic oscillations
- Conduction losses can be accounted for
- HF ripple can be estimated

7. Average Models


The Switched Inductor Model (SIM) Strategy

- Identify the switched assembly
- Replace the switching part by a continuous behavioral (analog) equivalent circuit
- Leave the analog part as-is
- Run the combined circuit on a general purpose simulator

The modeling methodology presented in this seminar is highly 'portable', independent of simulator


Demonstration by PSPICE Ver. 10.5 (Demo Edition)

The switched inductor model

 


- The problematic part : Switched Assembly
- Rest of the circuit continuous - SPICE compatible
- The objective : translate the Switched Assembly into an equivalent circuit which is SPICE compatible

Average Simulation of PWM Converters

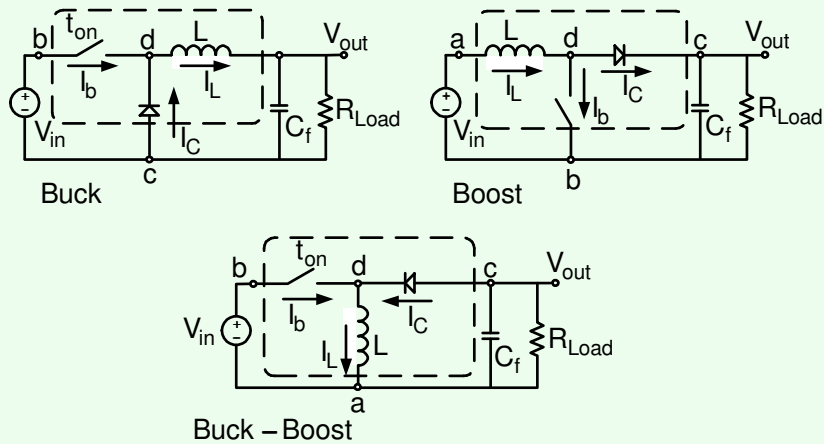


Possible switch modes

 


T_{ON} - switch conduction time
 T_{OFF} - diode conduction time
 T_{DCM} - no current time (in DCM)

The Switched Inductor Model (SIM) (CCM)


The concept of average signals

 

 Objective : To replace the switched part by a continuous network




Average current

 


Similarly :
 
$$\bar{I}_c = \frac{\bar{I}_L T_{OFF}}{T_S} = \bar{I}_L D_{off}$$



Toward a continuous model

 

G_a, G_b, G_c - current dependent sources

$$G_a \equiv \bar{I}_L$$


$$G_b \equiv \bar{I}_L \cdot D_{on}$$

$$G_c \equiv \bar{I}_L \cdot D_{off}$$


I_L derivation

$$\frac{dI_L}{dt} = \frac{V}{L} \Rightarrow \frac{d\langle I_L \rangle}{dt} = \frac{\langle V \rangle}{L}$$

 $\langle X \rangle = \bar{X} = \text{Average value}$




Average inductor voltage

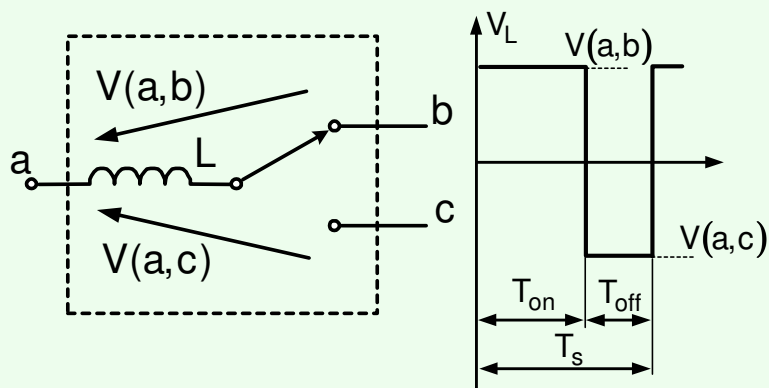

$$\begin{aligned} \bar{V}_L &= \frac{V(a,b) \cdot T_{on} + V(a,c) \cdot T_{off}}{T_s} = \\ &= V(a,b) \cdot D_{on} + V(a,c) \cdot D_{off} \end{aligned}$$

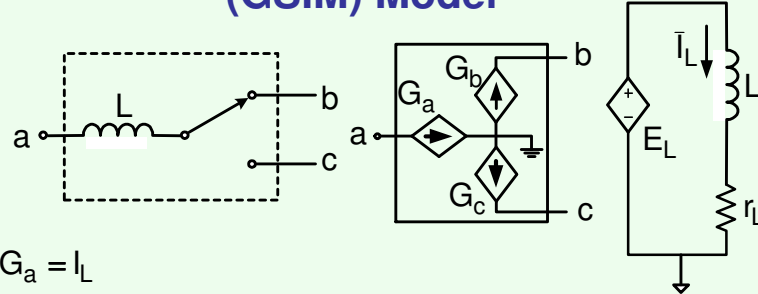The Generalized Switched Inductor Model (GSIM) Model



$$G_a = I_L$$

$$G_b = I_L \cdot D_{on}$$


$$G_c = I_L \cdot D_{off}$$

$$\bar{V}_L = V(a,b) \cdot D_{on} + V(a,c) \cdot D_{off}$$

Topology independent !

Example: Implementation in Buck Topology

1. The formal approach

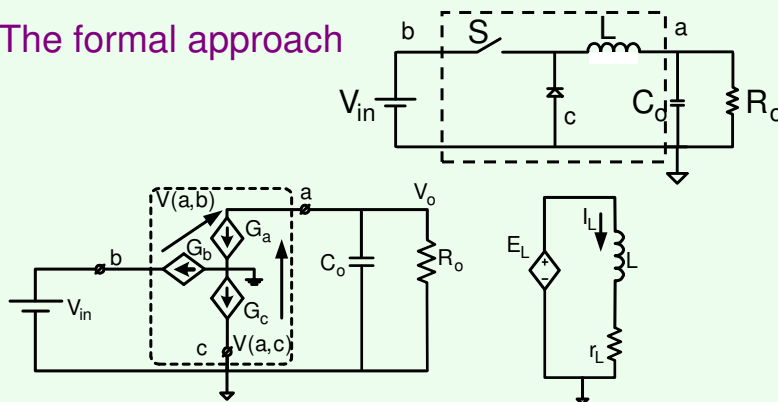


$$G_a = I(L) \quad G_b = I(L) \cdot D_{on} \quad G_c = I(L) \cdot D_{off}$$

$$E_L = [V_0 - V_{in}] \cdot D_{on} + [V_0 - 0] \cdot D_{off}$$


Implementation in Buck Topology

 2. The intuitive approach - by inspection




Polarity: (voltage and current sources) selected by inspection

Boost

 


- Emulate average voltage on inductor
- Create I_L dependent current sources

Making the model SPICE compatible

 

I_L and D_{ON} are time dependent Variables $\{I_L(t), D_{ON}(t)\}$
 D_{ON} is not an electrical variable

In SPICE environment

 

D_{on} is coded into voltage

Running SPICE simulation


DC (steady state points) - as is

TRAN (time domain) - as is


AC (small signal) - as is

- Linearization is carried out by simulator !

Discontinuous Model (DCM)

 


The combined DCM / CCM model

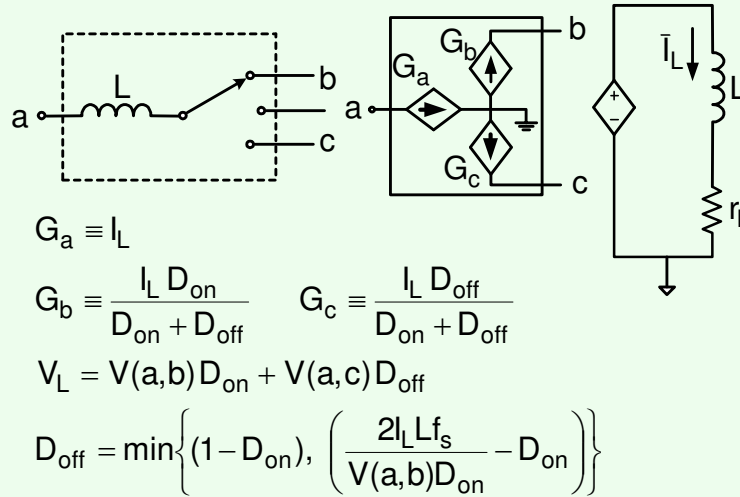

Synchronous Power Stages (diode replaced by switch)

- Only two states for switched inductor:
open and closed
- No third state as in DCM
- Use CCM model


Example: Buck Converter

 

File: Buck_cy_by_cy.OPJ

Cycle by Cycle simulation
of PWM Buck converter

buck_cy_by_cy.sch

 


PARAMETERS:
VIN = 10v


PARAMETERS:
LOUT = 75u
COUT = 220u
RLOAD = 10

PARAMETERS:
RESR = 0.07
RINDUCTOR = 0.1


PARAMETERS:
FS = 100k
TS = {1/fs}

 Power Start-Up at Constant D_{on} 

Zooming up

 


Average model

 


File: Buck.OPJ

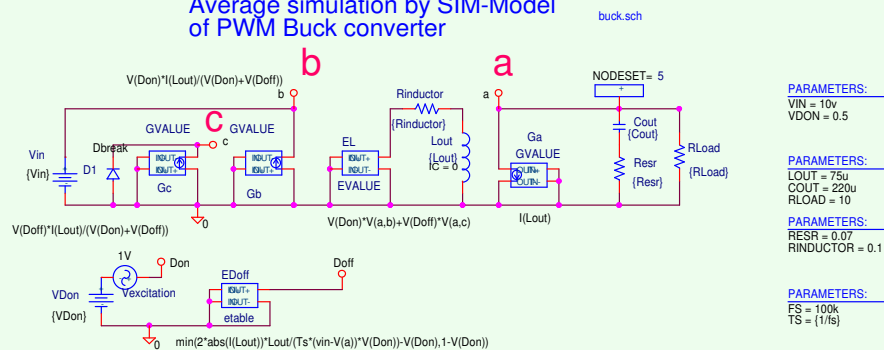Average simulation by SIM-Model
of PWM Buck converter




- D_{on} coded into voltage
- D_{off} for CCM/DCM


Inductor

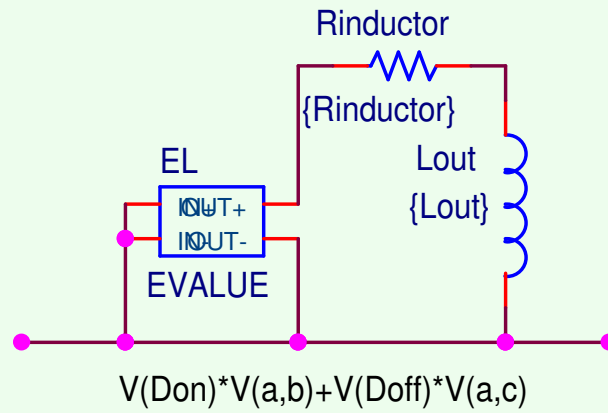


Input side

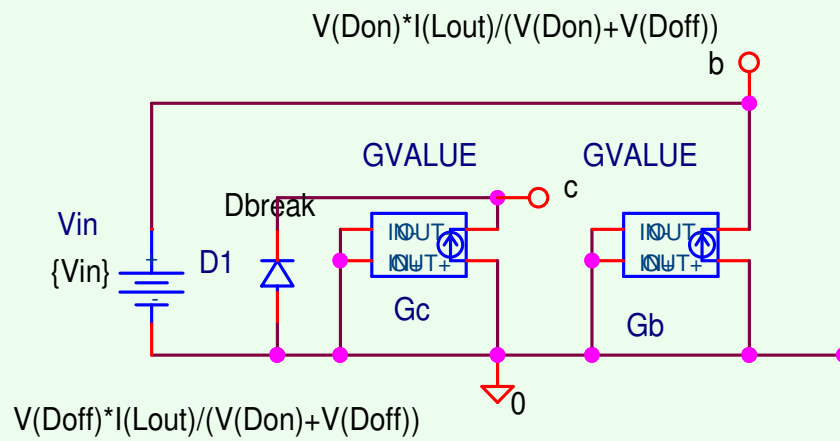


Output side

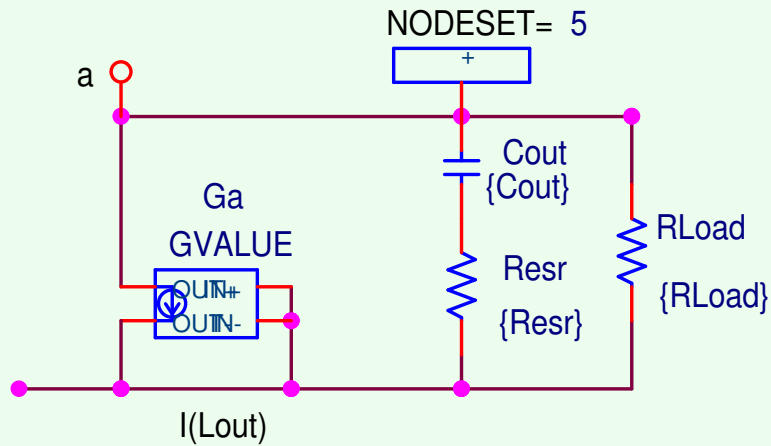


DC Sweep plus Parametric (on Rload)

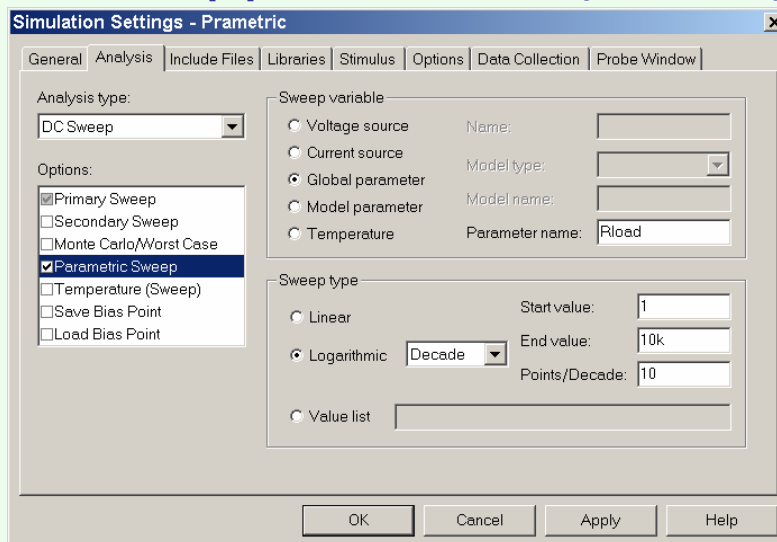


Sweeping R_{load} Constant D_{on}

 


Transient Analysis –Power Turn-On

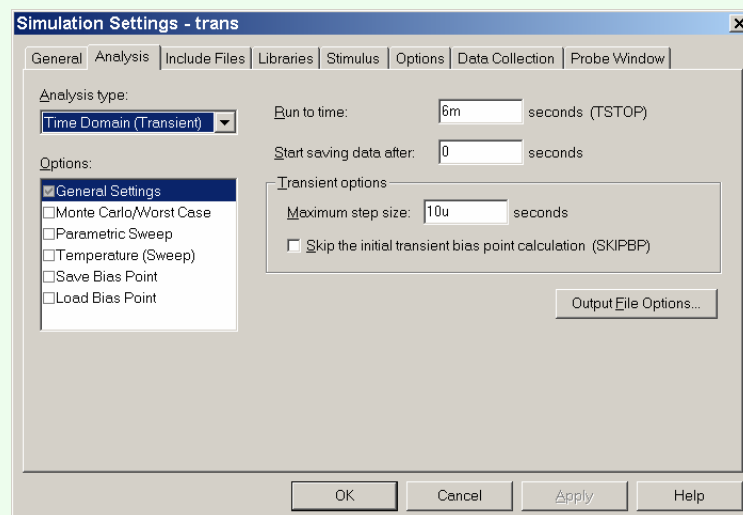

Power Start-Up at Constant D_{on}

 


 Comparing Cycle-by-Cycle to Average Simulation



AC Analysis

The Real Strength of Average Simulation

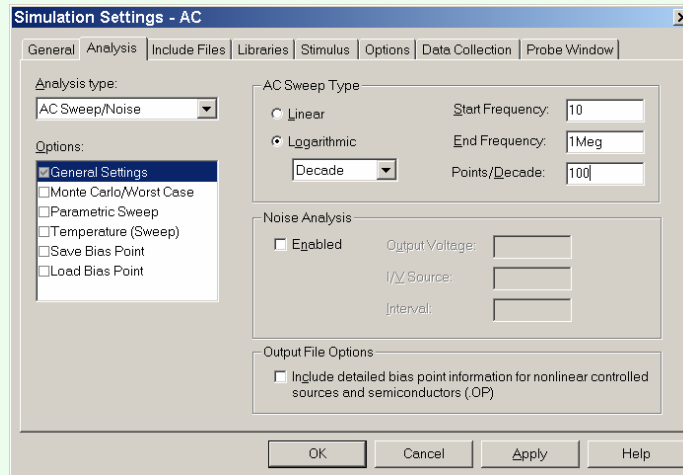

Linearization

- The circuit is linearized by simulator (elements, devices and expressions)
- Numerical linearization !
e.g. a source $f(x,y,z)$ is replaced by:

$$\begin{aligned} & \frac{f(X + \Delta X, Y, Z) - f(X, Y, Z)}{\Delta X} x \\ & + \frac{f(X, Y + \Delta Y, Z) - f(X, Y, Z)}{\Delta Y} y \\ & + \frac{f(X, Y, Z + \Delta Z) - f(X, Y, Z)}{\Delta Z} z \end{aligned}$$

- Transparent to user

PSpice simulations examples




Buck Average



Buck Cy by Cy



Boost

 

Boost Simulation


SIM-Model under CCM & DCM
for PWM Boost converter

Boost.sch

 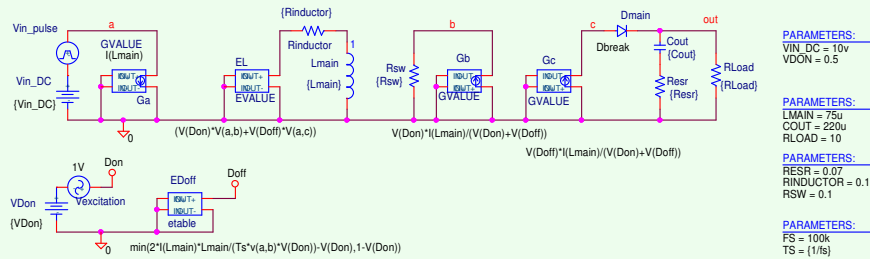

$$R_{Load} = 10\Omega$$

DCM

 


$$R_{Load} = 1000\Omega$$

PSpice simulation example



Boost simulation

Modulators – The Duty Cycle Generators

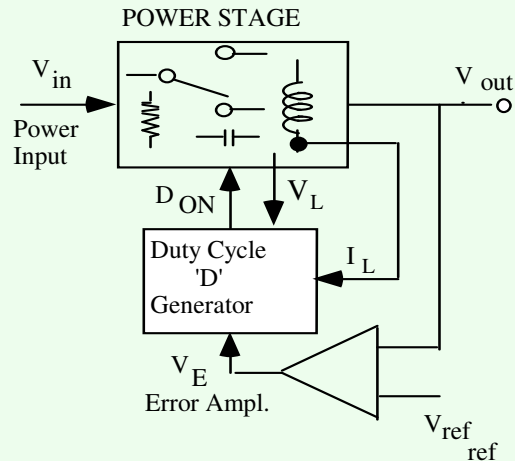


- General representation of a switch mode DC-DC converter


PWM MODULATOR - Voltage Mode

$$\frac{D}{V_e} = K_M (\text{voltage mode}) = \frac{V_E - V_M}{V_P - V_M}$$
 
$$\frac{d}{V_e} = \frac{v_e}{V_P \cdot V_M}$$



Coding

 



$$K_M (\text{voltage mode}) = \frac{V_E - V_M}{V_p - V_M}$$

D coded into voltage


$$0 \leq V_D \leq 1$$

Duty Cycle Limiter

- Behavioral dependent source ETABLE

  


Average Current Mode

 

- V_E is a function of V_o and I_L
- 'Control' is the original analog circuit
- Same modulator as in voltage mode

Peak Current Mode Control

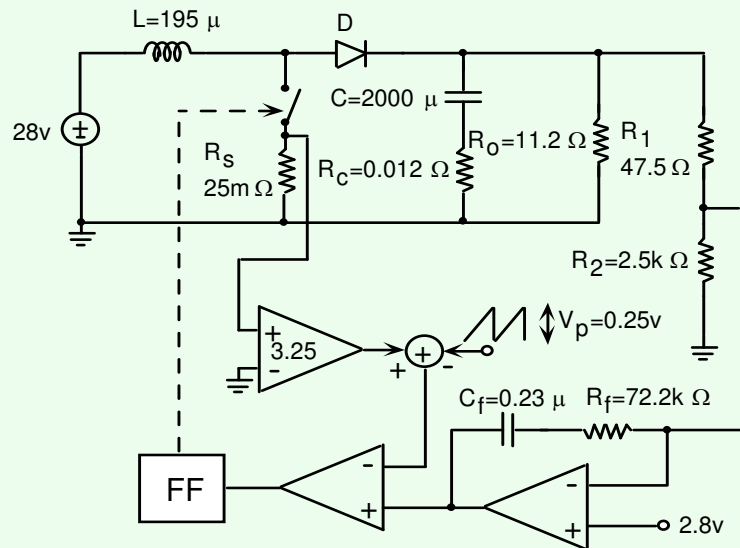

Current Mode CCM

$$EDon = \frac{V(Ve) - KS \frac{|I(L)|}{V(Don) + V(Doff)}}{TS \left(MC + KS \frac{V(a,b)}{2L} \right)}$$

$V(V)$

KS = Current Loop Gain

MC = Slope Compensation

TS = Switching Period

L = Inductance of main inductor


$|I(L)|$ = Average inductor current

If you can write an expression, it can be modeled !


SIM-Model under CCM & DCM
for Current-Mode PWM Boost converter

File: CM-Boost.opj

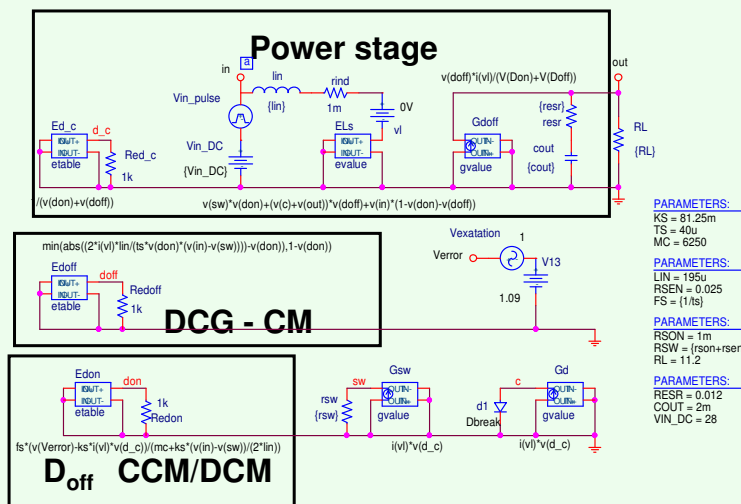Schematic file name: CM-Boost\CM-Boost.sch




Inductor

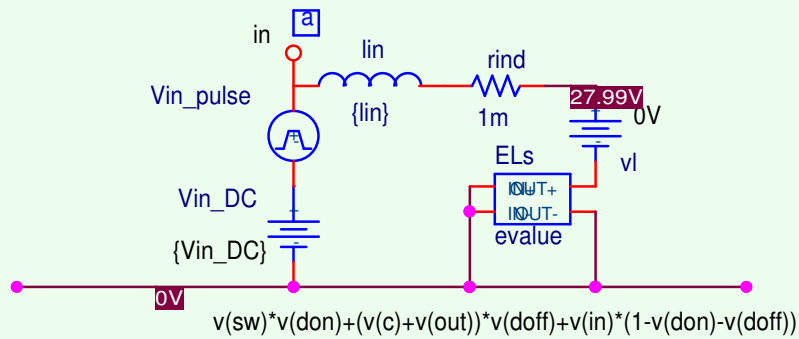


Duty Cycle Generator

 
$$\min(\text{abs}((2 \cdot i(vl) \cdot \text{lin} / (\text{ts} \cdot v(don)) \cdot (v(in) - v(sw)))) - v(don)), 1 - v(don))$$



0V

 
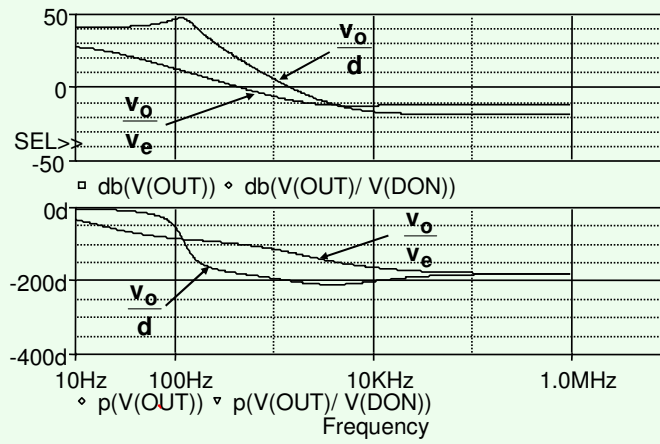
$$fs \cdot (v(Verror) - ks \cdot i(vl) \cdot v(d_c)) / (mc + ks \cdot (v(in) - v(sw)) / (2 \cdot \text{lin}))$$



$V(out)/V(Don)$ as normal
 $V(out)/V(Verror)$ lower order

PSpice simulation example



CM-Boost

Models of IC Controllers


- Vendors do not supply simulation models of IC controllers
- Large signal controllers' models are supplied with some simulators (e.g. PSIM)
- Average models (applicable for small signal analysis) are available from AEi
- It is easy to build your own behavioral average models (for control)

The Power Stage small-signal response

- A prerequisite for control design
- Can be obtained by analytical derivations/expressions
- By Simulation
 - On switched model (cycle by Cycle)
 - Average models

Feedback Loop Design of PWM Converters

 1. Find $A(f)$ of Power stage
2. Decide on f_0
3. Choose type of compensating network
4. Calculate feedback network




Make $|\beta A|$ as large as possible

The Relationship to PID


$$\begin{aligned}
 H(s) &= \frac{v_{\text{comp}}}{v_e} = K_p + \frac{K_I}{s} + s \cdot K_d = \\
 &= \frac{K_d \cdot s^2 + K_p \cdot s + K_I}{s} = \frac{K_d}{K_I} \frac{(s + \omega_{z1}) \cdot (s + \omega_{z2})}{s} \\
 \omega_{z1,2} &= \frac{-K_p \pm \sqrt{(K_p)^2 - 4K_d K_I}}{2K_d}
 \end{aligned}$$

The Relationship to PID

 
$$= \frac{K_d \cdot s^2 + K_p \cdot s + K_I}{s} = \frac{K_d}{K_I} \frac{(s + \omega_{z1}) \cdot (s + \omega_{z2})}{s}$$



The Relationship to PID

 

The Relationship to PID

 


BW Limitations (of LG, crossing of A and B)


- PWM is a sampled data system .
- Nyquist sampling theorem applies
- Cross over frequency f_o (A, B, LG) $< f_s/2$
- In practice $f_o < 10 f_s/2$

 8. Analog compensator networks


Possible phase compensation schemes Lag (A)




$$A_o = \frac{R_f}{R_{in}}$$

 

Lag (B)

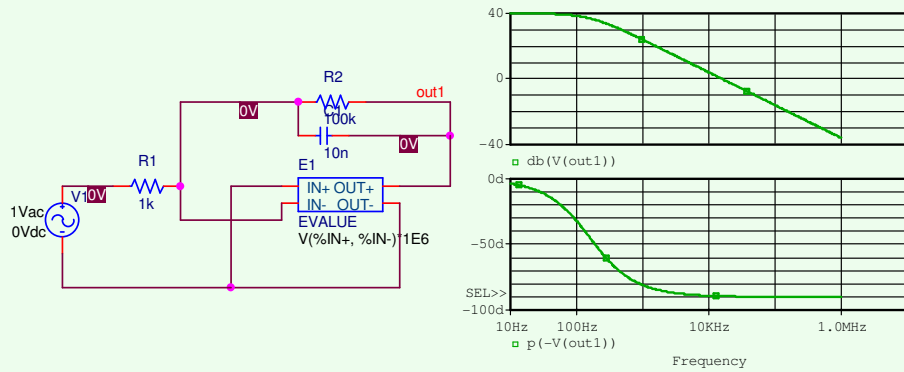


Lag – Lead (B)

 


$$A_0 = A_{OL}(\text{ampl.})$$

$$f_L = \frac{1}{2\pi C_f R_f}$$


$$A_2 = \frac{R_f}{R_{in}}$$

 


Lag-Lead (B)

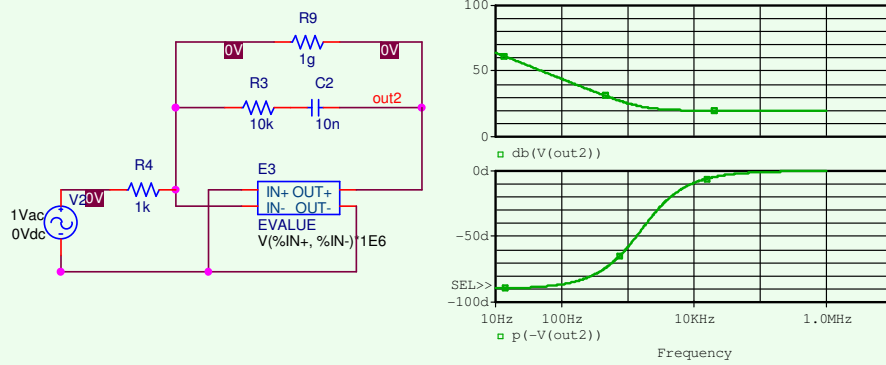


Double zero compensation scheme

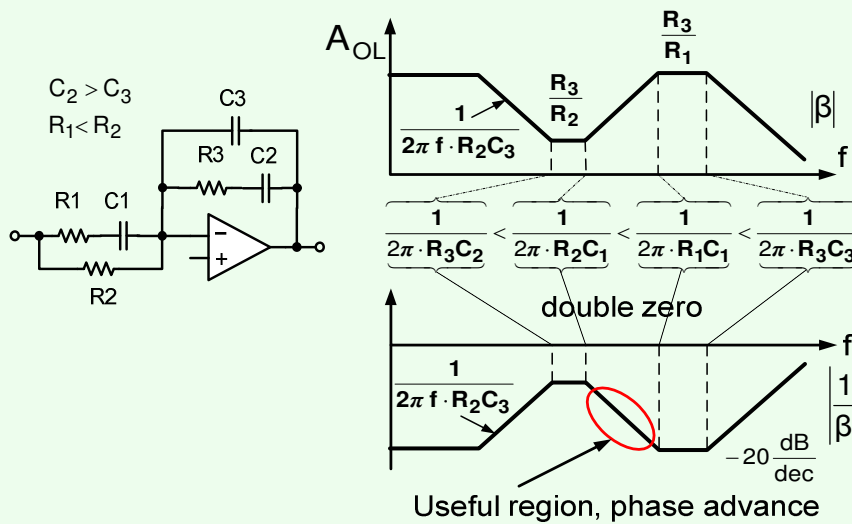


Double Zero (B)

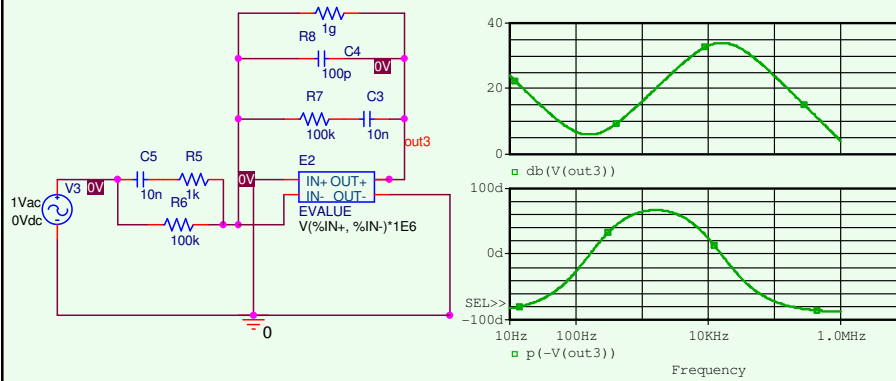

Double Zero- Alternative

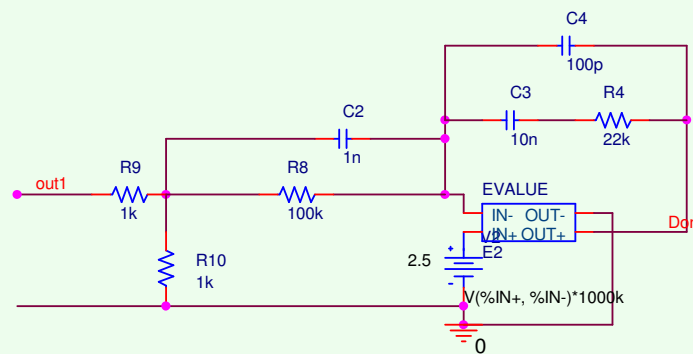

Application of Double Zero Compensator

 


Voltage Mode Control Compensator Design Example




VM Regulator

Obtaining the Loop Gain by Simulation

 


$$LG = \frac{S_f}{S_\epsilon}$$

Loop Gain by Simulation

 

$$LG = \frac{S'_f}{S'_\epsilon}$$


Loop Gain by Simulation

 

$$LG = \frac{S'_f}{S'_\epsilon}$$

Loop-Gain

 Getting Loop-Gain under closed loop response $\{A(f)*B(f)\}$



$$LG(f) = V1/V2$$

Rules for Getting Loop-Gain by Simulation

The relevant analysis is .AC


- Locate the AC source at the output of a low impedance device (could be real or behavioral)
- Set the AC value to any value (1 V is fine)
- Make sure that there are no other AC sources in the system
- Check bias point (.OUT file)
- Remember that the classical stability criteria take into account the phase reversal (180°)

PSpice Simulation




VM Regulator


PSIM Demonstration

 


Peak and Average Current Mode

 

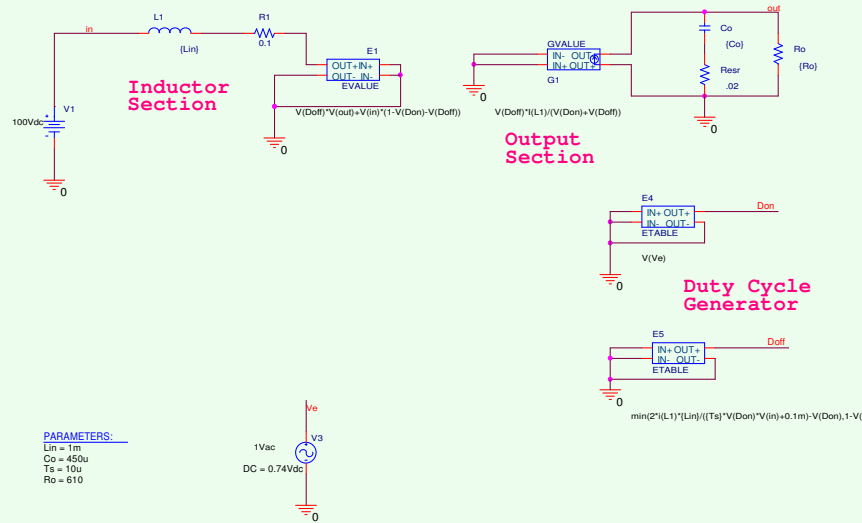
- Two step design: inner loop and outer loop




The response for inner loop design


 


$F=13\text{kHz}$; Gain= -13.3db=0.22

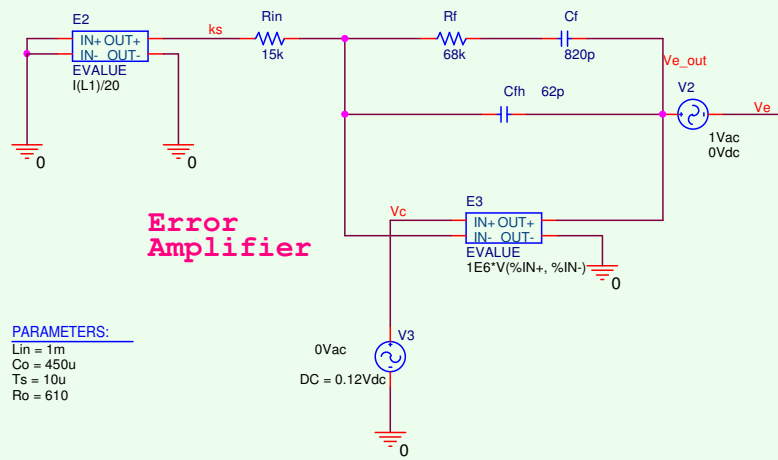


- The error amplifier (For $K_S = 1/20$)

 

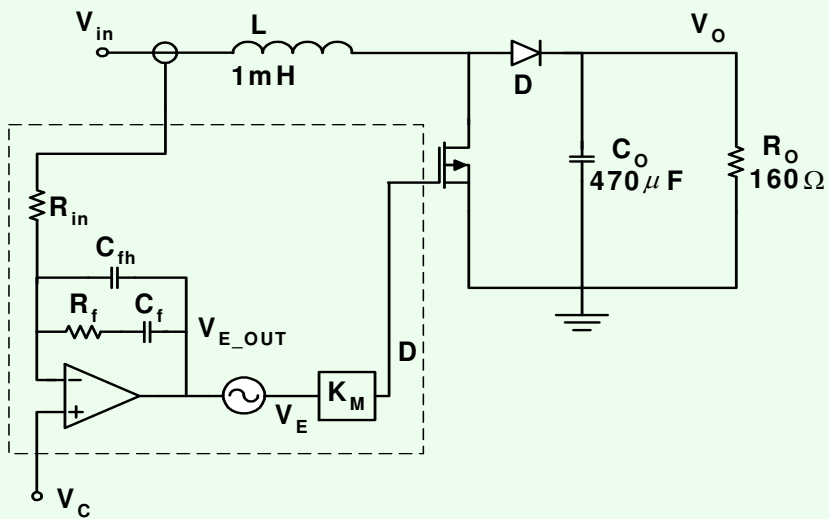 


$V_{ac} = 1 \text{ V}$; $V_c = \text{Constant (operating point)}$; $K_S = 1/20$

LoopGain

 


Phase margin 60°

Nyquist Plot

 


• Imaginary(LG) versus Real(LG)


Nichols Plot

 

- |LG| versus Phase(LG)


Closed Inner Loop (Tracing)

 

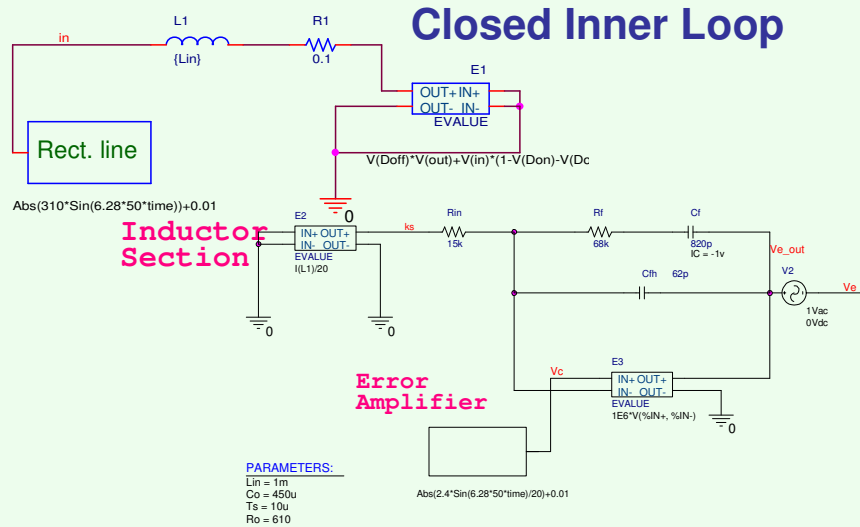


- Toward Power factor Correction (open loop)

Transient Simulation -CCM

 


In CCM: $D_{on} + D_{off} = 1$


After changing L_m to $300\mu H$

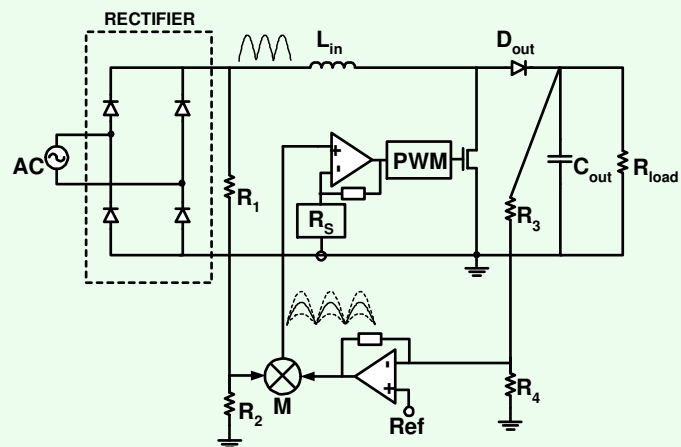


UC3854 Based Average Model

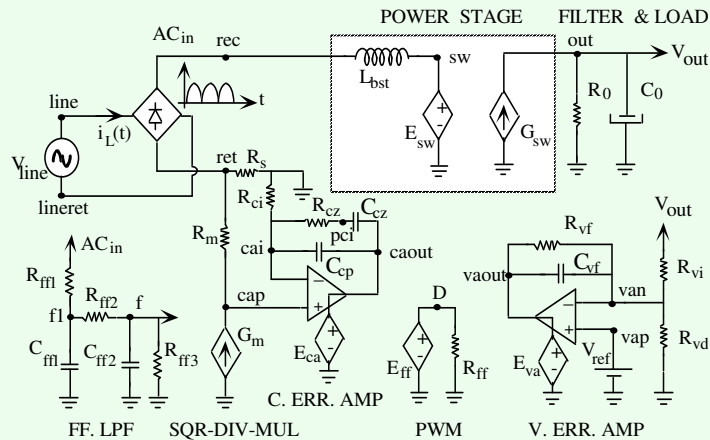


CCM - Based on UC3854

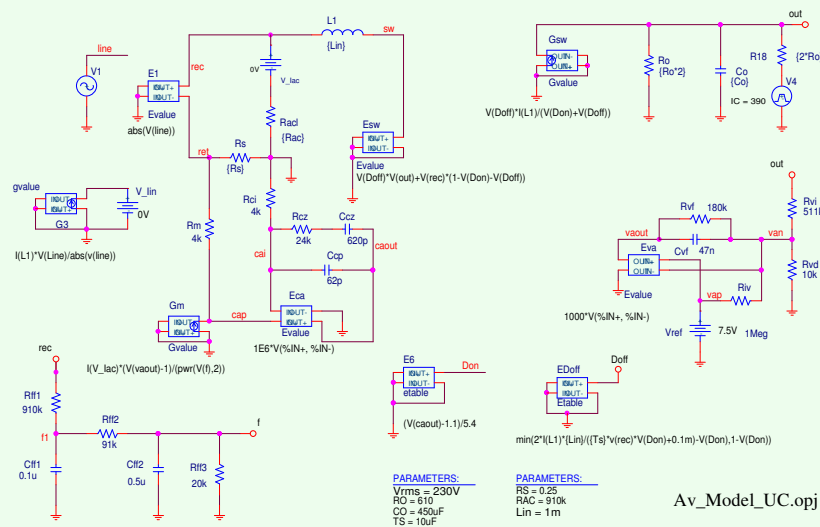

Voltage Control Loop

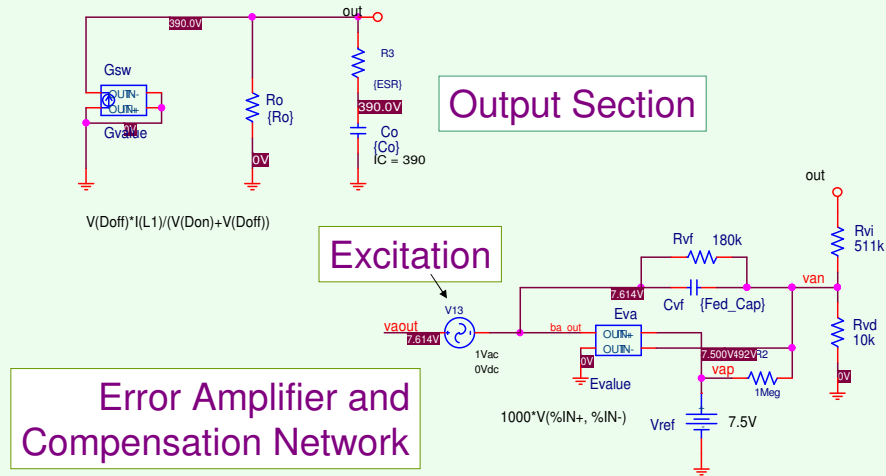


 Input Voltage Step Response: 115Vrms to 230Vrms




$P_{out}=250W$, Slew Rate=160V/mS

 Input Voltage Step Response: 115Vrms to 230Vrms




$P_{out}=250W$, Slew Rate=160V/mS

 Current Loop Gain at Different Input Voltages



$V_{in}=50V, 100V, 200V, 300V$

Loop Gain of Voltage Control Loop

 

PSpice simulation




PFC-AC




PFC-TRAN

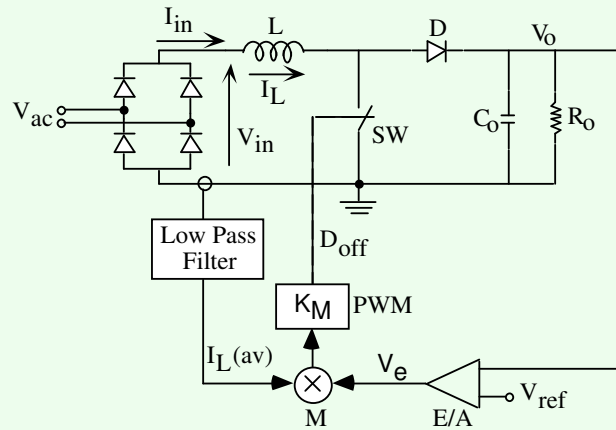
CCM Control Concept with no Sensing of Input Voltage



Average Model

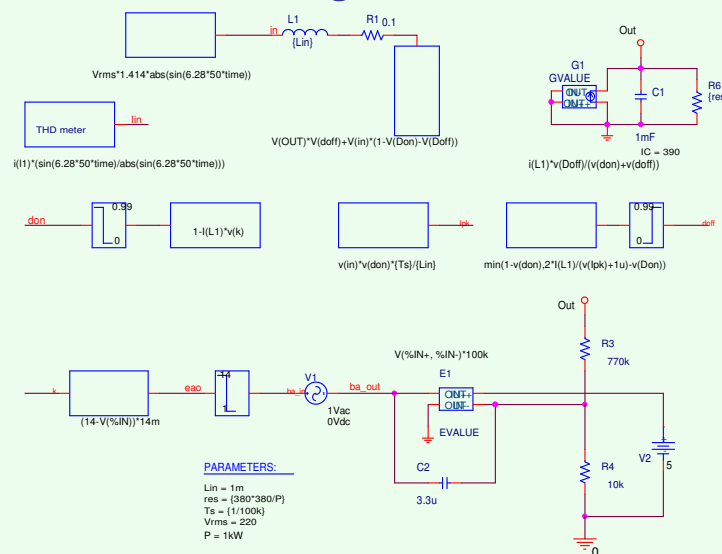


 Input Behavior at Different Line Voltages




$P_{out}=1kW$, $V_{in}=80V_{rms}$, $230V_{rms}$, $265V_{rms}$

Loop Gain of Current Control Loop

 

Current Loop Transfer Function

 



PSpice simulation




PFC_no_sens-AC



PFC_no_sens-TRAN

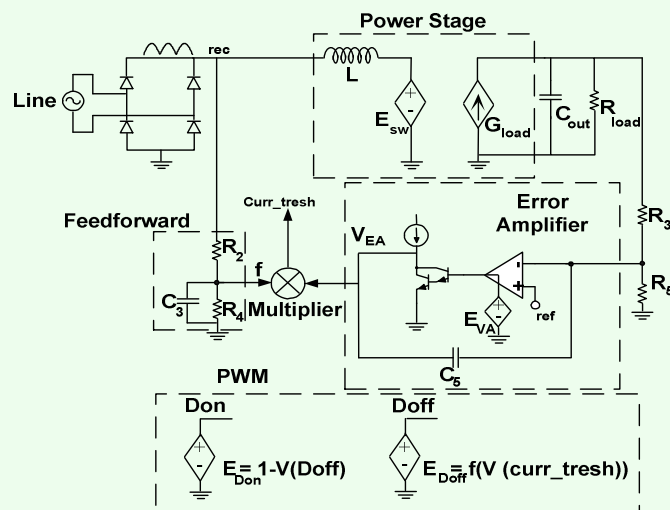 

MC33261 Based Average Model

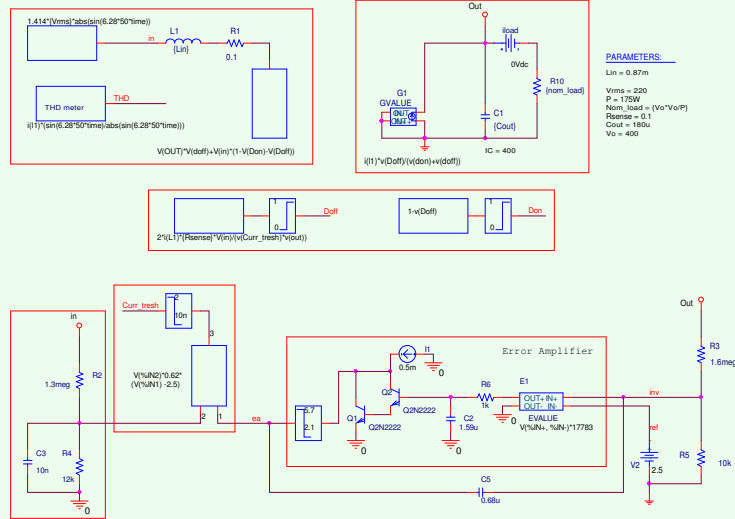

PSpice simulation




PFC_bord-AC




PFC_bord-TRAN

 
Border Line Control Concept with no Sensing of Input Voltage




Principle of Operation

 


MC33260 Based Average Model

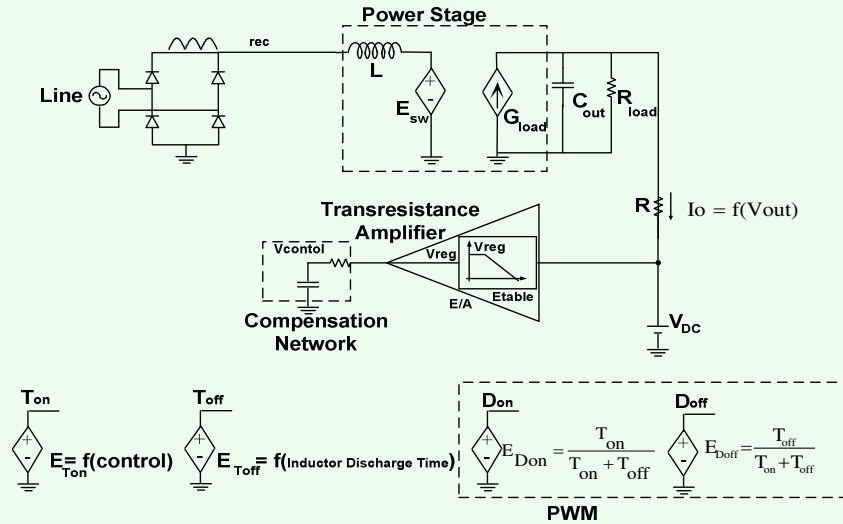


MC33260 Based Average Model

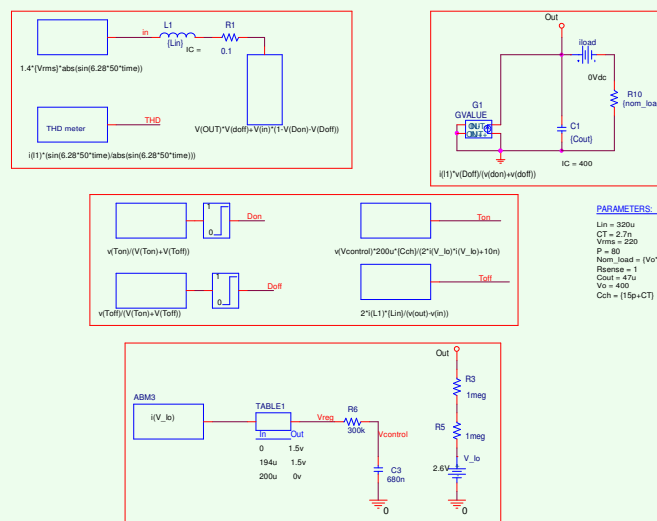

Combined Stage (Boost-Flyback)


 


Principle of Operation

 


- C_B serves as output capacitor for Boost Section and as input voltage source for Flyback section.

Average Model

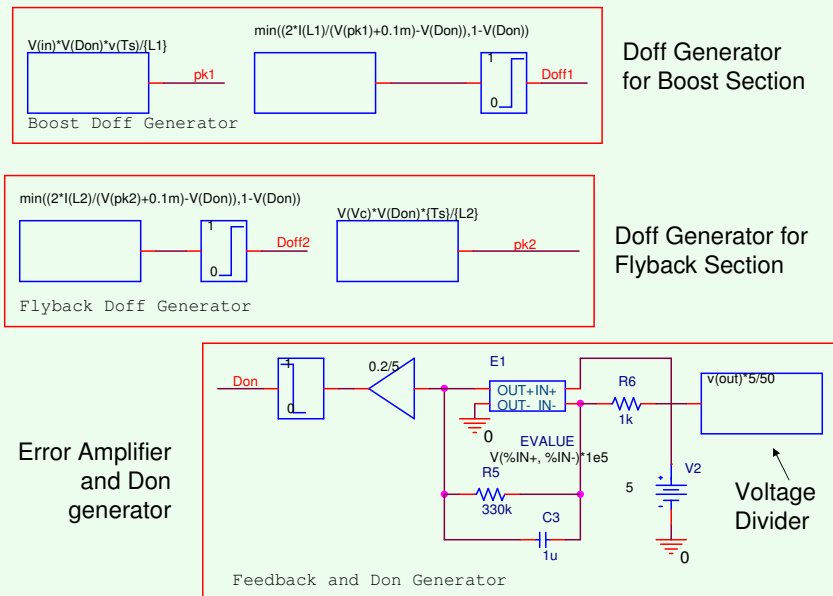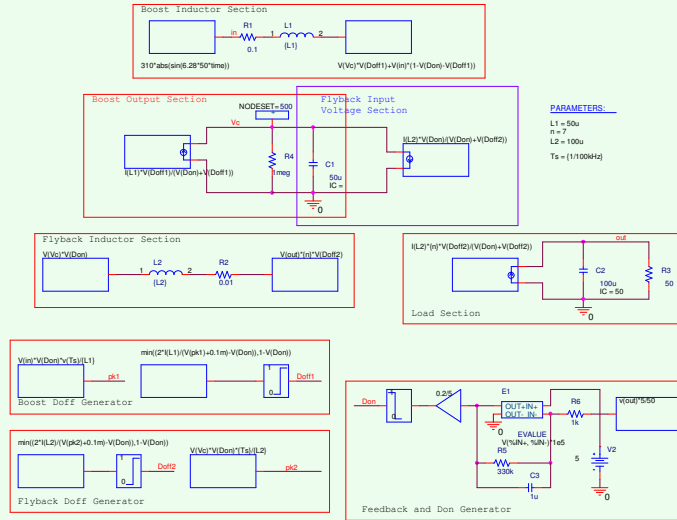


Behavior at Different Power Levels

 


Vin=230V, Pout=100W, 50W

Combined Stage (SEPIC with Transformer)

 


Principle of Operation

ON:

 


BOOST

 


FLYBACK


OFF:

 

Average Model

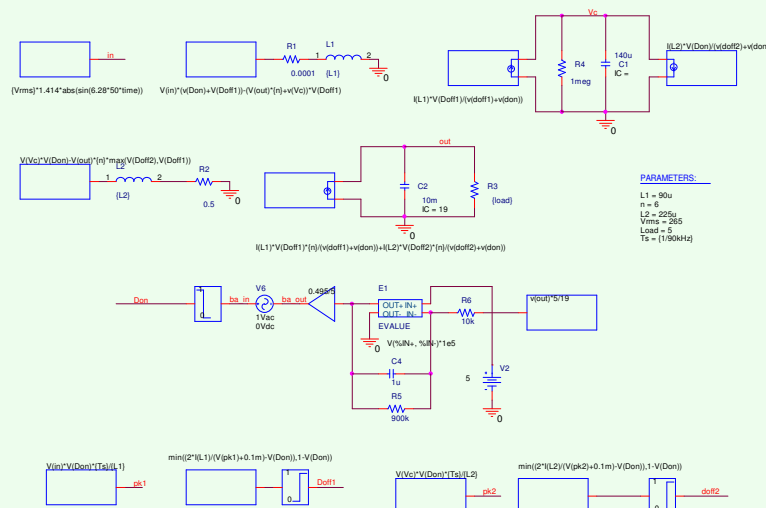

Behavior at Different Power Levels

 

Vin=230V, Pout=70W, 50W

PSpice simulation




PFC_DCM - avg



PFC_DCM - CBC


9. Digital Control

Analog/continuous control

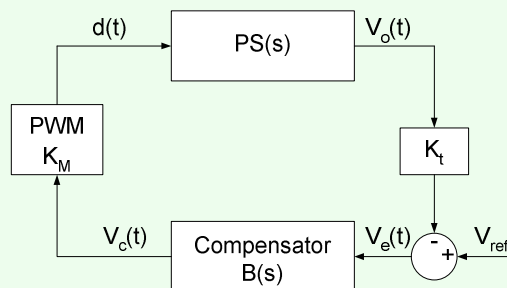

$$LG(s) = K_t K_M PS(s) B(s)$$


Digital/discrete control

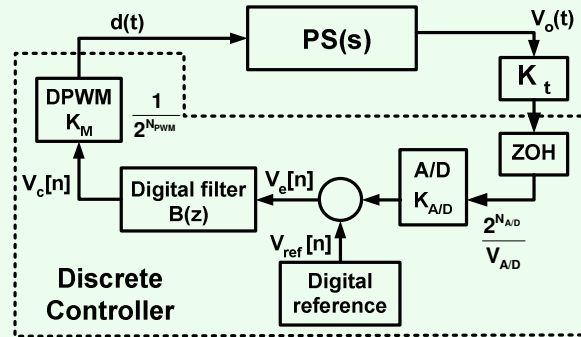

$$LG = K_t K_M K_{A/D} e^{-s\Delta T} PS(s) B(z) \quad e^{-s\Delta T} \Leftrightarrow \frac{1}{z}$$


- Sampling and computation delay
- Additional gain – $K_{A/D}$

Sampling Issues ZOH

 


ZOH

$f_s = 10\text{KHz}$

 


Sampling Delays

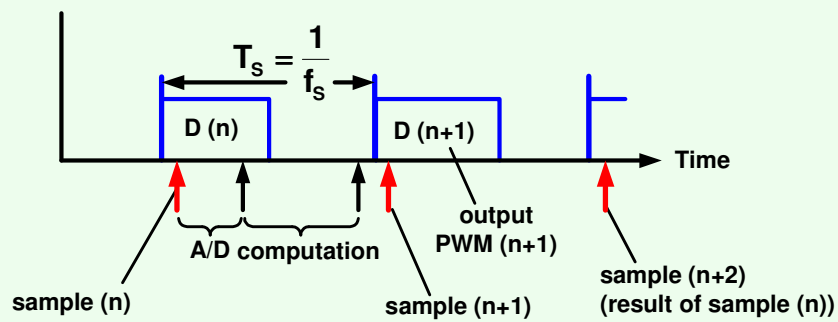


Sampling rate = f_s

Slow Sampling Rate

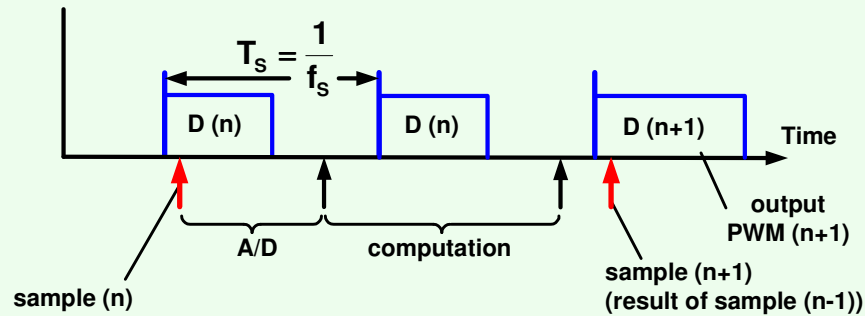

$$\text{Sampling rate} = \frac{f_s}{2}$$

Compensation network, continuous

 

$$K = \frac{R_1}{R_2}$$

$$\tau = R_1 C$$

$$\frac{V_e(t)}{R_2} = -C \frac{dV_c(t)}{dt} - \frac{V_c(t)}{R_1}$$


Differential equation: $-KV_e(t) = \tau \frac{dV_c(t)}{dt} + V_c(t)$

Integral equation: $-K \int V_e(t) dt = \tau \int dV_c(t) + \int V_c(t) dt$

Laplace transform: $-\frac{K}{s} V_e(s) = \tau V_c(s) + \frac{1}{s} V_c(s)$

Transfer function: $\frac{V_c(s)}{V_e(s)} = -\frac{K}{s\tau + 1}$

Discretization rules

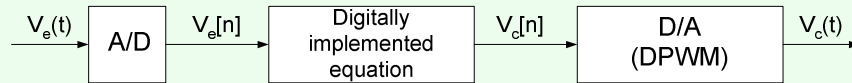

Differential equations transforms to difference equations

$$\frac{dV(t)}{dt} \Rightarrow \frac{V[n] - V[n-1]}{\Delta T}$$


Integral equations transforms to summations

$$\int V(t)dt \Rightarrow \Delta T \sum_{k=-\infty}^{n-1} V[k]$$

Z-transform is the discrete time dual of the Laplace transform

$$V(s) = \int_{-\infty}^{\infty} V(t)e^{-st}dt \Leftrightarrow V(z) = \sum_{k=-\infty}^{\infty} V[k]z^{-k}$$

Transfer functions are represented in Z

 

$$\frac{V_o}{V_e} = \frac{1}{z+a} = \frac{z^{-1}}{1+az^{-1}}$$

$$V_o(1+az^{-1}) = V_e z^{-1}$$

$$V_o = V_o(n-1) \cdot a + V_e(n-1)$$

Unstable if $a > 1$

The intuitive meaning of the z operator

$s \Rightarrow$ derivative operator; $z \Rightarrow$ Delay operator

$$\frac{V_o}{V_{in}}(z) = \frac{z}{z^2 - 1}$$

$$\frac{V_o}{V_{in}}(z) = \frac{z^{-1}}{1 - z^{-2}}$$

$$V_o(1 - z^{-2}) = V_{in} z^{-1}$$

$$V_o = V_o z^{-2} + V_{in} z^{-1}$$

$$V_o = V_o(n-2) + V_{in}(n-1)$$

Continuous to discrete transformation

- Pole-Zero matching
- Zero Order Hold (ZOH)
- Trapezoid (bilinear) transformation

Pole-Zero matching

- Map discrete poles/zeros by $z_i = e^{s_i \Delta T}$
- For complex s-domain roots $s_i = a_i + jb_i \rightarrow z_i = e^{a_i \Delta T} e^{jb_i \Delta T}$
- Maintain same DC gain $G(s)|_{s=0} = G(z)|_{z=1}$

$$\frac{V_c(s)}{V_e(s)} = \frac{K}{s\tau + 1} \xrightarrow{z} \frac{KP}{z - e^{-\Delta T/\tau}}$$

$$\left(a_i = \frac{1}{\tau}; b_i = 0 \right)$$


$$\frac{V_c(s)}{V_e(s)} \Big|_{s=0} = \frac{V_c(z)}{V_e(z)} \Big|_{z=1} \rightarrow P = 1 - e^{-\Delta T/\tau}$$

$$\frac{V_c(z)}{V_e(z)} = \frac{K(1 - e^{-\Delta T/\tau})}{z - e^{-\Delta T/\tau}} = \frac{m}{z - n}$$

m, n - constants

Zero Order Hold (ZOH)

Hold equivalent = sampled area

 


$$s \Leftrightarrow \frac{z-1}{\Delta T}$$

$$\frac{V_c(s)}{V_e(s)} = \frac{K}{s\tau + 1}$$


$$\frac{V_c(z)}{V_e(z)} = \frac{K}{\frac{z-1}{\Delta T}\tau + 1}$$

Transfer function:
 
$$\frac{V_c(z)}{V_e(z)} = \frac{K\Delta T}{\Delta T + \tau} \left(\frac{1}{z - \frac{\tau}{\Delta T + \tau}} \right) = \frac{m}{z - n}$$



Trapezoid (bilinear) transformation

 


$$\frac{V_c(s)}{V_e(s)} = \frac{K}{s\tau + 1} \quad s \Leftrightarrow \frac{2}{\Delta T} \frac{z-1}{z+1}$$


Transfer function:

$$\frac{V_c(z)}{V_e(z)} = \frac{K}{\frac{2\tau}{\Delta T} \frac{z-1}{z+1} + 1}$$
 
$$\frac{V_c(z)}{V_e(z)} = \frac{K \Delta T / 2}{\tau + \Delta T / 2} \left(\frac{z+1}{z-1} \right)$$




Comparison of hold types

 

$f_s = 50\text{KHz}$

$$\frac{V_c(s)}{V_e(s)} = \frac{10}{0.1s + 1}$$


Effects of sampling rate

 

Hold Type: ZOH

Discretization:
Inherent Phase-lag

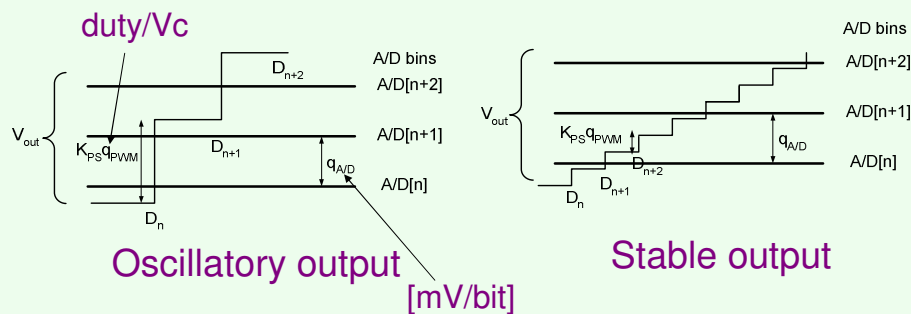A/D and PWM Resolution The Limit Cycle Problem



No Limit cycle rules

One bit of the DPWM should change V_o
by less than 1 bit of the A/D

Taking into account the system gains

$$K_{PS}K_t q_{DPWM} < q_{A/D}$$

Compensator must include integral action
(included in PID)

System must satisfy Nyquist criterion

$$1 + A(s)B(s) > 0$$

Stability

$$1 + A(s)B(s) \neq 0$$

Oscillations

Digital Compensator Design Methods

- Frequency domain based
- Pole location in z plane
- Time domain design

Frequency domain design

1. Design a frequency domain controller (Bode, Nichols, etc.)
2. Refinement: take into account the sampling and computational delays
3. Translate the analog controller into a Z equivalent
4. Simulate by numerical simulator (e. g. MATLAB)

Frequency domain design References

- [1] V. Yousefzadeh, W. Narisi, Z. Popovic, and D. Maksimovic, "A digitally controlled DC/DC converter for an RF power amplifier", *IEEE Trans. on PE*, Vol. 21, 1, 164-172, 2006.
- [2] G. F. Franklin, J. D. Powell, M. L. Workman, *Digital control of dynamic systems*, 3rd edition, Prentice Hall, 1998.
- [3] B. J. Patella, A. Prodic, A. Zirger, and D. Maksimovic, "High-frequency digital PWM controller IC for DC-DC converters", *IEEE Trans. on PE*, Vol. 18, 1, 2, 438-446, 2003.

Z Plane Design Using the MATLAB SISO tool

1. Define the system structure
2. Define the Plant response
3. Define the compensator template
4. Select the analysis view (Root Locus, Bode, Nichols)
5. Insert design constraints (gain, BW, PM, settling time, Natural frequency, etc.)
6. You can use the GUI to change pole/zero locations (either in S or Z and observe the resulting closed loop response)

- Trial and error procedure

MATLAB SISO tool References

- [1] O. Garcia, A. de Castro, A. Soto, J. A. Oliver, J. A. Cobos, J Cezon, "Digital control for power supply of a transmitter with variable reference", *IEEE Applied Power Electronics conference APEC-2006*, 1411-1416, Dallas, 2006.
- [2] The Mathworks, Matlab control toolbox user guide, available at www.mathworks.com.

Time domain Discrete Controller Design

- Digital compensator operates in the sampled-data domain
- Direct controller design - does not involve errors related to approximations (s to z)
- When working in the time domain, system attributes such as bandwidth and phase margin seem artificial
- Relevant parameters are: rise time, overshoot etc.
- Improved performance of the closed loop system compared to other discrete design approaches
- Does not involve trial and error procedure


Time domain Discrete Controller Design References

- [1] G. F. Franklin, J. D. Powell, M. L. Workman, Digital control of dynamic systems, 3rd edition, Prentice Hall, 1998.
- [2] J. R. Ragazzini and G. F. Franklin, Sampled-data control systems, McGraw-Hill, 1958.
- [3] J. G. Truxal, Automatic feedback control systems synthesis, McGraw-Hill, 1955.
- [4] B. Miao, R. Zane, and D. Maksimovic, "Automated Digital Controller
- [5] Design for Switching Converters", *IEEE Power Electronics Specialists Conference, PESC-2005*, 2729-2735, Recife, 2005.
- NEW** [6] M. M. Peretz and S. Ben-Yaakov, Time domain design of digital compensators for PWM DC-DC converters, *IEEE Applied Power Electronics conference APEC-2007*, In Press.


Time domain Discrete Controller Design

- Plant transfer function (continuous): $A(s)$
- S to Z transformation: $A(s) \rightarrow A(z)$
- Defining the desired closed loop response: $A_{CL}(s)$
- S to Z transformation: $A_{CL}(s) \rightarrow A_{CL}(z)$
- Ideal controller:
 
$$A_{CL}(z) = \frac{A(z)B(z)}{1 + A(z)B(z)} \rightarrow B(z) = \frac{A_{CL}(z)}{1 - A_{CL}(z)} \frac{1}{A(z)}$$



Closed-loop response

 

$$45^\circ < \varphi_m < 90^\circ$$

2nd order system

$$\frac{1}{\frac{s^2}{\omega_n^2} + \frac{s}{\omega_n Q} + 1}$$

Design constraint:
System will have the
characteristic equation


Describing the closed-loop response by time domain characteristics

2nd order system

$$\frac{V_o(s)}{d(s)} = \frac{1}{\frac{s^2}{\omega_n^2} + \frac{s}{\omega_n Q} + 1}$$

Rise time: $t_r \approx \frac{1.8}{\omega_n} \Rightarrow \omega_n \approx \frac{1.8}{t_r}$

 Overshoot $M_p = e^{-\frac{\pi}{2Q} / \sqrt{1 - \frac{1}{4Q^2}}} \Rightarrow Q = -\frac{\sqrt{1 + \left(\frac{\ln(M_p)}{\pi}\right)^2}}{2 \frac{\ln(M_p)}{\pi}}$



Describing the desired A_{CL} in Z

- Second order characteristic equation sets the $A_{CL}(z)$ denominator (a_0, a_1, a_2)

$$\frac{s^2}{\omega_n^2} + \frac{s}{\omega_n Q} + 1 \xrightarrow{z} \frac{b_0 z^2 + b_1 z + b_2}{a_0 z^2 + a_1 z + a_2}$$

- To derive the complete A_{CL} equation (i. e. numerator) additional constraints are to be satisfied:
- Stability at infinity (bounded system) $A_{CL}(z)|_{z=\infty} = 0$
- Steady state error to step $A_{CL}(z)|_{z=1} = 1$
- Response to ramp (velocity constant) $\frac{dA_{CL}(z)}{dz} \Big|_{z=1} = \frac{1}{K_V}$

Template-oriented controller

- Ideal controller to satisfy the design constraints

$$B(z)_{\text{ideal}} = \frac{A_{\text{CL}}(z)}{1 - A_{\text{CL}}(z)} \frac{1}{A(z)}$$


This design method suffers from:

- controller implementation on digital platform vary by design (plant, A_{CL} , etc.)
- High order - too many parameters – long computation time

Template-based controller

- In each computational event, only data points around the sampling instant are considered
- The controller uses only information that is in the vicinity of the sampling instant and is blind to all other information
- The implemented finite difference equation can be based on a short-term time response of the system rather than on the full response

 A look at the step response of $B(z)_{ideal}$



Objective:

- Find a compensator template that will match (or will be close to) the ideal response – at least at the first few samples
- The compensator should have fewer computation cycles

The answer - PID controller

PID template: continuous

$$\frac{V_c(s)}{V_e(s)} = \frac{\frac{s^2}{\omega_c^2} + \frac{s}{\omega_c Q} + 1}{s}$$

PID template: discrete p-z matching

$$\frac{V_c(z)}{V_e(z)} = \frac{a + bz^{-1} + cz^{-2}}{z^{-1} - z^{-2}}$$


Taking into account the sampling delay (A/D)

$$\frac{V_c(z)}{V_e(z)} = \frac{a + bz^{-1} + cz^{-2}}{1 - z^{-1}}$$

PID controller


Difference Equation (will be implemented on the digital platform)
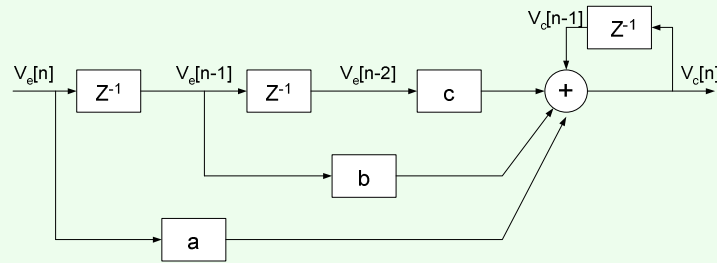
$$V_c[n] = V_c[n-1] + aV_e[n] + bV_e[n-1] + cV_e[n-2]$$



Only 3 samples!!!
Only 4 computations!!!



Extracting PID coefficients (a, b, c)

 


PID coefficients extraction procedure

$$V_c[n] = V_c[n-1] + aV_e[n] + bV_e[n-1] + cV_e[n-2]$$
  
$$\begin{aligned} n=0 & \begin{cases} V_c[0] = V_c[-1] + aV_e[0] + bV_e[-1] + cV_e[-2] \end{cases} \\ n=1 & \begin{cases} V_c[1] = V_c[0] + aV_e[1] + bV_e[0] + cV_e[-1] \end{cases} \\ n=2 & \begin{cases} V_c[2] = V_c[0] + aV_e[2] + bV_e[1] + cV_e[0] \end{cases} \end{aligned}$$



Design example

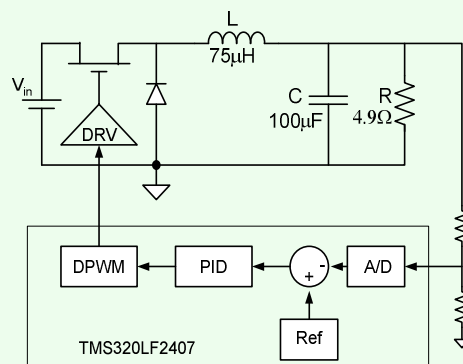



$V_o = 5V$ Switching frequency=sampling rate= 50KHz

$T_r=100\mu$

$M_p=10\%$


$$A_{CL}(z) = \frac{0.5044z + 0.4123}{z^2 - 1.403z + 0.4956}$$

Plant response

  


$$PS(s) = \frac{3.333 \cdot 10^8}{s^2 + 2500s + 1.333 \cdot 10^8} \quad \xrightarrow{\text{ZOH}} \quad PS(z) = \frac{0.06548z + 0.06459}{z^2 + 1.908z + 0.96}$$

Ideal controller response

 


$$B(z) = \frac{0.5044z^3 - 1.375z^2 + 1.271z - 0.3958}{0.06548z^3 - 0.1249z^2 + 0.05945z}$$


Extracting PID coefficients (a, b, c)

 

Closed loop response

 


Closed loop step response - results

 

- Reference is stepped from 5V to 6V


A look at the frequency domain

 

PM=40

BW=4KHz

Experimental

 

PM=33

BW=3.2KHz


Load step

PID coefficients

$a=3.4$

$b=-6.15$

$c=2.93$

 

Slower Response


Switching frequency=sampling rate= 50KHz

$V_o = 5V$

$T_r=500\mu$


$M_p=0\%$ No over shoot

Controller response

 


Derived PID: $B(z)_S = \frac{1.52 - 2.81z^{-1} + 1.38z^{-2}}{1 - z^{-1}}$

Closed loop

 


Closed loop step response - results

 

- Reference is stepped from 5V to 6V


A look at the frequency domain

 

PM=80

BW=800Hz

Experimental

 

PM=80

BW=1.5KHz


Load step

PID coefficients


$a=1.52$

$b=-2.81$

$c=1.38$

 


Comparison to analog design

 


The analog controller was set to have the same bandwidth as the digital design

Load step applied: 1A to 1.5A


Load step - analog (Spice simulation)

 

Load step - analog

 

Load step digital

 

Thank you for Your Attention

**Thanks to the Israeli Science Foundation for
supporting our research**


10. Q&A

Sort Biography of Presenter Prof. Shmuel (Sam) Ben-Yaakov

- BSc degree in Electrical Engineering from the Technion, Haifa Israel, in 1961
- MS and PhD degrees in Engineering from the UCLA, in 1967 and 1970 respectively.
- Full Professor at the Department of Electrical and Computer Engineering, Ben-Gurion University of the Negev, Beer-Sheva, Israel,
- Heads the Power Electronics Group of BG University
- Published over 250 scientific and technical papers in leading journals and conferences
- Holds about 20 patents (as an inventor)
- Consultant to companies worldwide on design-oriented theoretical issues in the areas of analog and power electronics as well as on product development.
- Founder and CTO of Green Power Technologies Ltd. (<http://www.g-p-t.com>)
- Present research interests include: power electronics aspects of piezoelectric elements, analog and digital control, power factor correction, lighting electronics, soft switching and active thermal cooling.

Primary to secondary isolation

The problem :

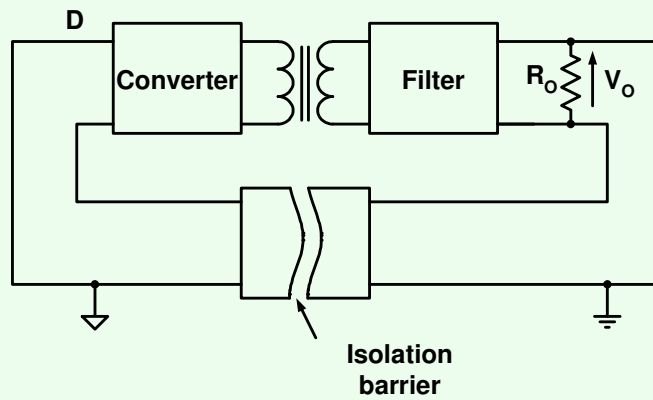

Alternative

